
Chapter 5

Sequential Logic Circuits

Clock Signal

 


Fig. 5.1 Clock signal.

Rise/Fall Time

 


Fig. 5.2 Rise time and fall time.

Sequential Circuit

 


Fig. 5.3 General structure of a sequential logic circuit.

Asynchronous Sequential Circuit

 


Fig. 5.4 General structure of an asynchronous sequential circuit.

Asynchronous Sequential Circuit

 


Fig. 5.5 Inverter connected into an asynchronous sequential logic circuit.

Oscillating Inverter

 


Fig. 5.6 Oscillation of an inverter with its output connected to its input.

Ring Oscillator

 


Fig. 5.7 Ring oscillator consisting of 5 inverters.

Inverter Loop

 


Fig. 5.8 Non-inverting loop formed by two inverters.

Operating Point

 


Fig. 5.9 Operating points of a CMOS memory element.



999999-11
XYZ 10/28/02

D-Latch

 


Fig. 5.11 An alternative D-latch utilizing a pMOS transistor.

D-Latch

 


Fig. 5.12 Behavior of the D-latch.

Sequential Circuit

 


Fig. 5.13 Sequential logic circuit employing D-latches.

Clock


 


Fig. 5.14 Clock signal for the sequential logic circuit in Fig. 5.13.

 

Negative-Edge-Triggered FF



 


Fig. 5.16 Behavior of a negative-edge-triggered D-flip-flop.

Flip-Flops

 

Negative edge-triggered flip-flop

 

Positive edge-triggered flip-flop

Fig. 5.17 Symbols of flip-flops.

Sequential Circuit

 


Fig. 5.18 Sequential circuit incorporating D-flip-flops.

Clock Design

 


Fig. 5.19 Timing diagram for the design of an edge-triggering clock.

Sequential Circuit

 


Fig. 5.20 Sequential circuit with two stages of combinational logic.

Two-Phase Non-Overlapping Clock

 


Fig. 5.21 Two-phase, non-overlapping clock signals.

Clock Overlapping

 


Fig. 5.22 Overlapping between ϕ and $\bar{\phi}$.

Stable Signal

 


Fig. 5.23 Output Q of a latch controlled by ϕ_1 .

Clock Signal Assignment

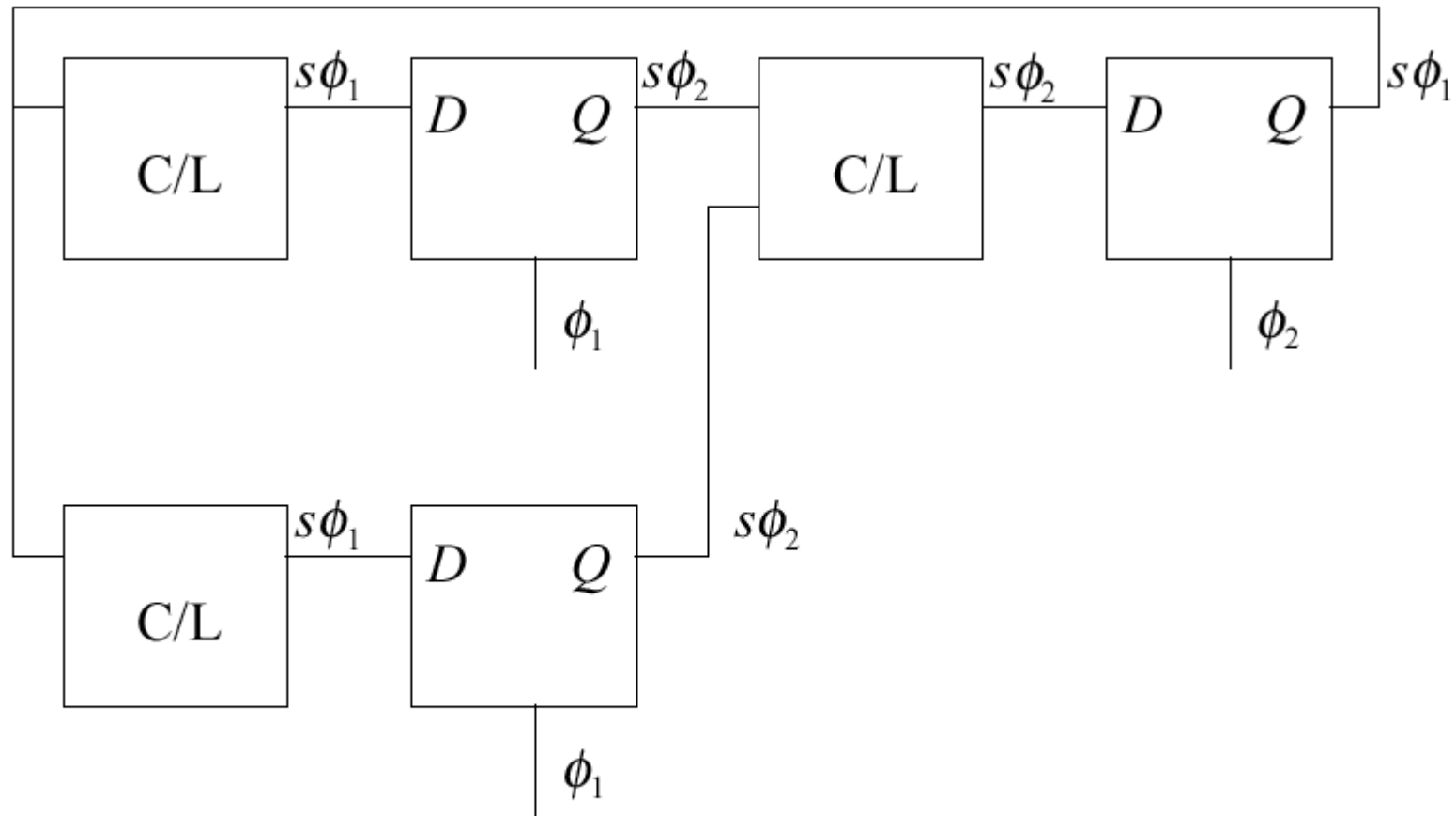


Fig. 5.24 Assignment of clock signals.

Two-Phase Non-Overlapping Clock

 


Fig. 5.25 Design of a two-phase, non-overlapping clock system.

Retiming

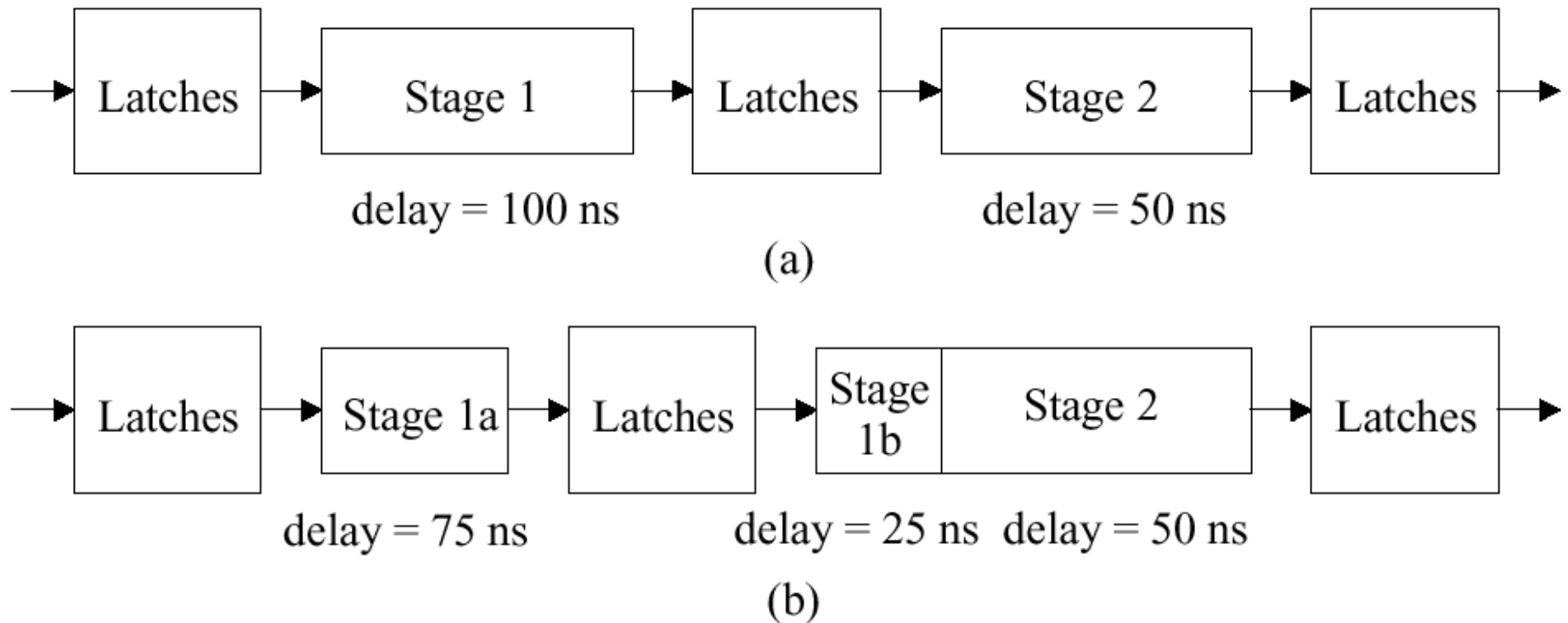


Fig. 5.26 Retiming example.

Clock Routing

 


Fig. 5.27 H-tree clock routing scheme.

Robot Lawn Mower

 


Fig. 5.28 Illustration of the robot lawn mower.

Mobile Robot

Sensor	Signal	Meaning	
Light	x	0: dark	1: bright
Obstacle	y	0: obstacle free	1: obstacle detected

Fig. 5.29 The sensor signals and their meanings.

Mobile Robot

<i>pq</i>	Left motor	Right motor	Robot
00	off	off	stops
01	off	on	turns left
10	on	off	turns right
11	on	on	goes straight

Fig. 5.30 Relations between control signals and robot movements.

Mobile Robot

 


Fig. 5.31 Mealy machine state diagram for the mobile robot controller.

Mobile Robot

State	Meaning
00	Next obstacle will be avoided by turning left
01	Turning left
11	Next obstacle will be avoided by turning right
10	Turning right

Fig. 5.32 States of the mobile robot controller.

Mobile Robot

	$xy = 0-$	$xy = 10$	$xy = 11$
s_1s_0	S_1S_0pq	S_1S_0pq	S_1S_0pq
00	0000	0011	0101
01	0000	1111	0101
11	0000	1111	1010
10	0000	0011	1010

Fig. 5.33 State table for the mobile robot controller.

Mobile Robot

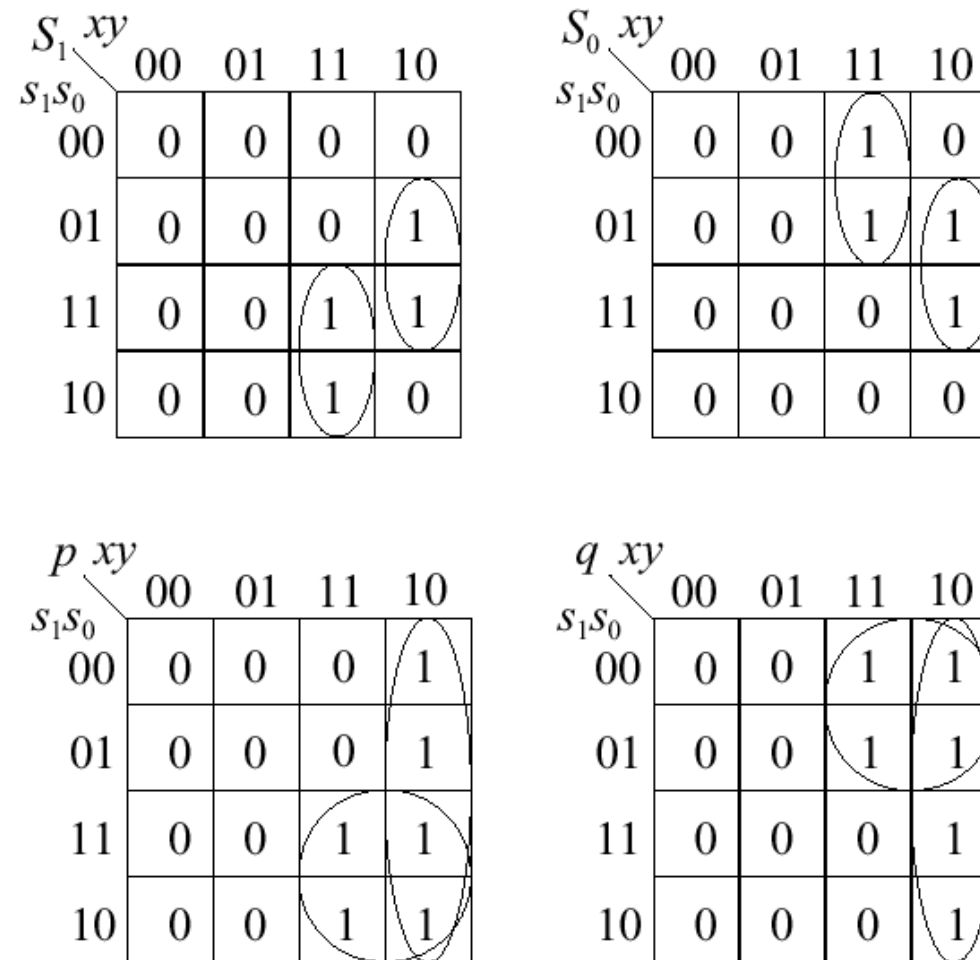


Fig. 5.34 Knaugh maps for mobile robot controller design.

Mobile Robot

 


Fig. 5.35 Block diagram for the mobile robot controller circuit.

64-Bit Adder

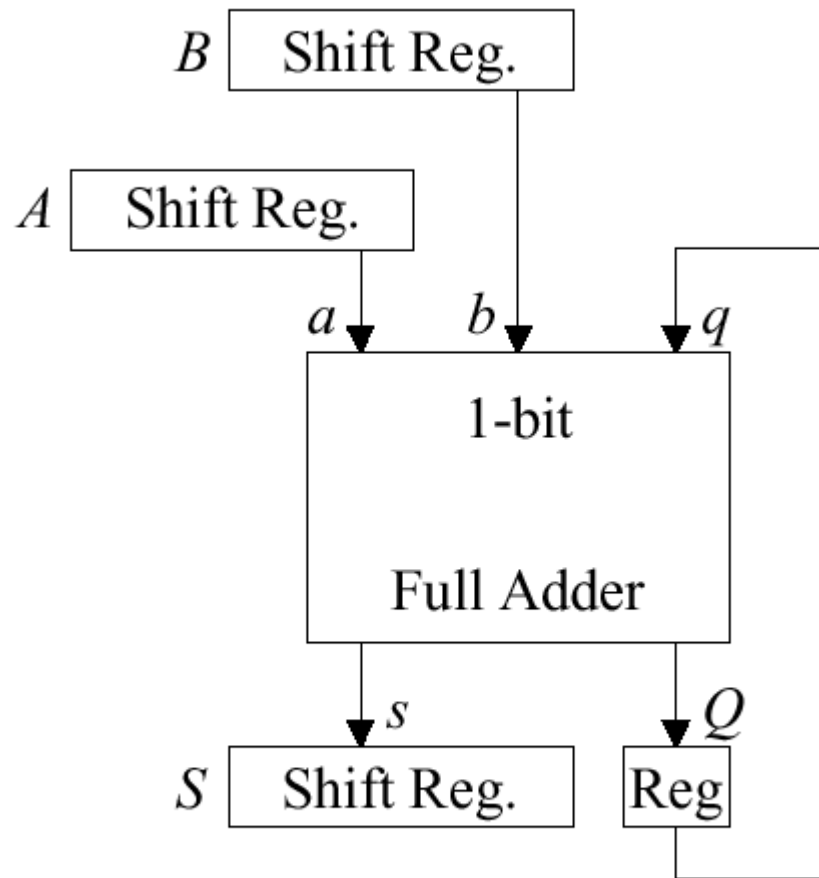


Fig. 5.36 64-bit adder.

Candy Machine

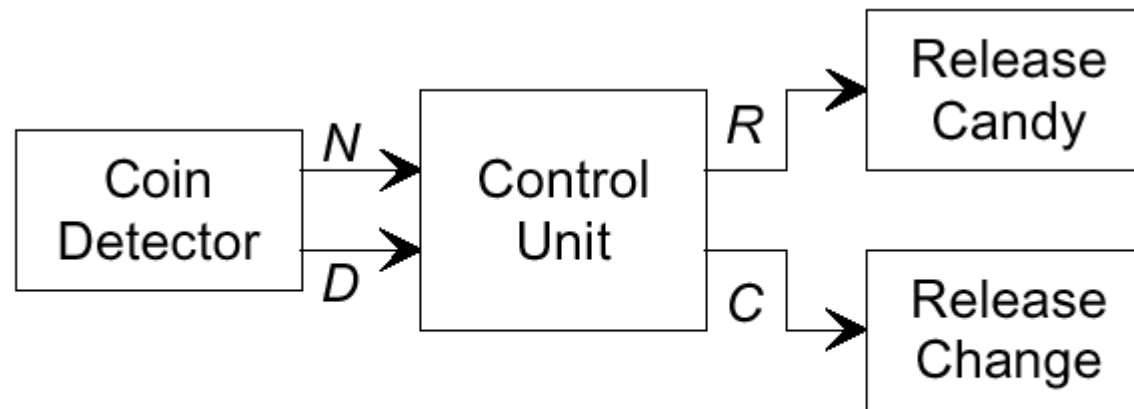


Fig. 5.37 Block diagram of a candy machine.

Candy Machine

 


Fig. 5.38 State diagram for a candy machine.