
Chapter 2

CMOS Logic Circuits

NMOS Transistor

 


Fig. 2.1 Physical structure and circuit symbol of an nMOS transistor.

NMOS Symbol

 


Fig. 2.2 Simplified nMOS transistor symbol.

NMOS Model

 


Fig. 2.3 Circuit for deriving the nMOS switch model.

NMOS Switch

 


Fig. 2.4 Two operating modes of the digitally controlled nMOS switch model.

PMOS Transistor

 


Fig. 2.5 Physical structure and circuit symbol of a pMOS transistor.

PMOS Symbol

 


Fig. 2.6 Simplified pMOS transistor symbol.

PMOS Switch

 


Fig. 2.8 Two operating modes of the digitally controlled pMOS switch model.

MOSFET Switches

v_I	Logic Level	nMOS	pMOS
V_{DD}	1	ON	OFF
V_{SS}	0	OFF	ON

Fig. 2.9 Switch model of MOSFETs

NMOS and PMOS

 


Fig. 2.10 Complementary relationship between nMOS and pMOS transistors.

Inverter

A	Z
0	1
1	0

 


Fig. 2.11 Truth table and logic symbol of an inverter.

Inverter Pull-Up

 


Fig. 2.12 Pull-up path of an inverter: (a) $A = 0$; (b) $A = 1$.

Inverter Pull-Down

 


Fig. 2.13 Pull-down path of an inverter: (a) $A = 0$; (b) $A = 1$.

Inverter

 


Fig. 2.14 Switch network implementing an inverter: (a) $A = 0$; (b) $A = 1$.

Inverter

 


Fig. 2.15 CMOS inverter.

CMOS Logic Structures

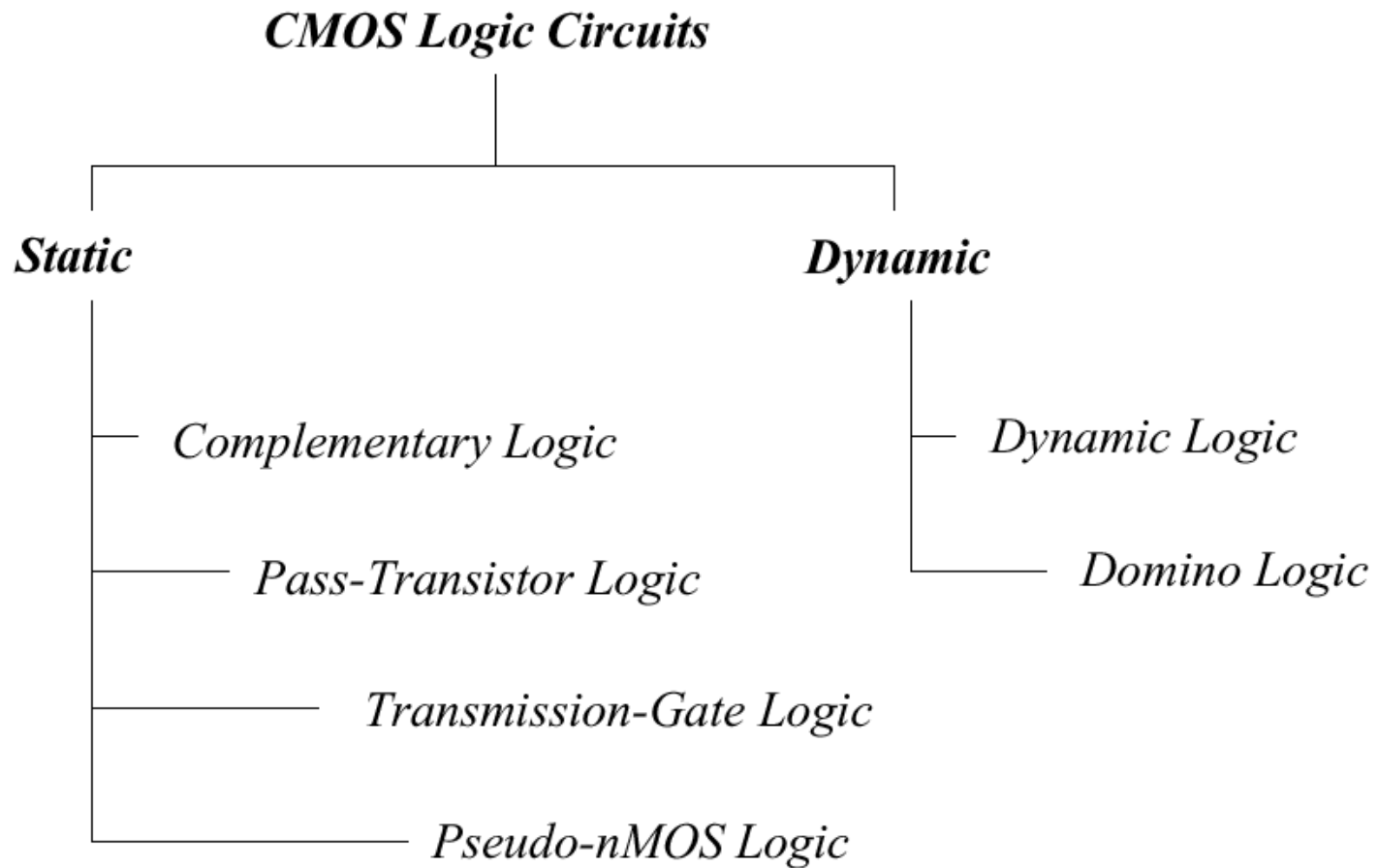


Fig. 2.16 Different structures of CMOS logic circuits.

Complementary Logic

 


Fig. 2.17 General structure of CMOS complementary logic circuit.

Serial Network

 


Fig. 2.18 Serial switch network.

Parallel Network

 


Fig. 2.19 Parallel switch network.

NMOS Output

 


Fig. 2.20 Output connected to V_{DD} through an nMOS transistor.

PMOS Output

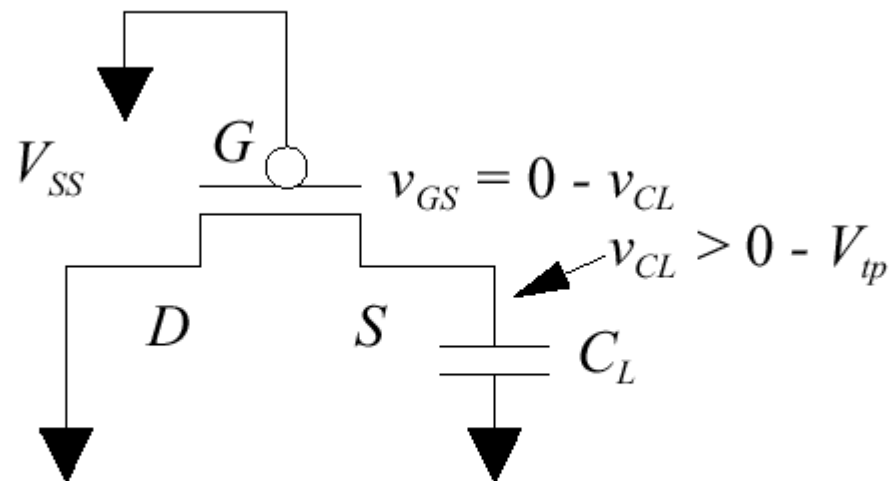


Fig. 2.21 Output connected to V_{SS} through a pMOS transistor.

Logic Swing

 


Fig. 2.22 Full logic swing and reduced logic swing.

NAND Pull-Up Network

 


Fig. 2.24 Pull-up network for $F = \overline{AB}$.

NAND Pull-Down Network

 


Fig. 2.25 Pull-down network for $F = \overline{AB}$.

NAND Gate

 


Fig. 2.26 Transistor schematic diagram of a two-input NAND gate.

Pull-Up and Pull-Down Networks

Pull-up network	Pull-down network
pMOS transistor	nMOS transistor
serial connection	parallel connection
parallel connection	serial connection

Fig. 2.27 Complementary pull-up and pull-down networks in a logic circuit.

NOR Gate

 


Fig. 2.28 Logic symbol of a two-input NOR gate.

NOR Pull-Up Network

 


Fig. 2.29 Pull-up network for $F = \overline{A + B}$.

NOR Gate

 


Fig. 2.30 CMOS two-input NOR gate.

Example 2.3

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Fig. 2.31 Truth table of F in Example 2.3.

Example 2.3

		AB			
		00	01	11	10
CD	00	1	1	0	1
	01	1	1	0	1
	11	1	1	0	0
	10	1	1	0	1

Fig. 2.32 Karnaugh map of F in Example 2.3.

Example 2.3

<i>Pull-down</i>		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	<i>Off</i>	<i>Off</i>	<i>On</i>	<i>Off</i>
	01	<i>Off</i>	<i>Off</i>	<i>On</i>	<i>Off</i>
	11	<i>Off</i>	<i>Off</i>	<i>On</i>	<i>On</i>
	10	<i>Off</i>	<i>Off</i>	<i>On</i>	<i>Off</i>

Fig. 2.33 Karnaugh map for the pull-down network in Example 2.3.

Example 2.3

<i>Pull-up</i>		<i>AB</i>			
		00	01	11	10
<i>CD</i>	00	On	On	Off	On
	01	On	On	Off	On
	11	On	On	Off	Off
	10	On	On	Off	On

Fig. 2.34 Karnaugh map for the pull-up network in Example 2.3.

Logic Circuit

 


Fig. 2.35 Logic circuit for function $F = \overline{A(B + CD)}$.

Example 2.4

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	1	1	1	1

Fig. 2.36 Karnaugh map of F in Example 1.4.

Example 2.4

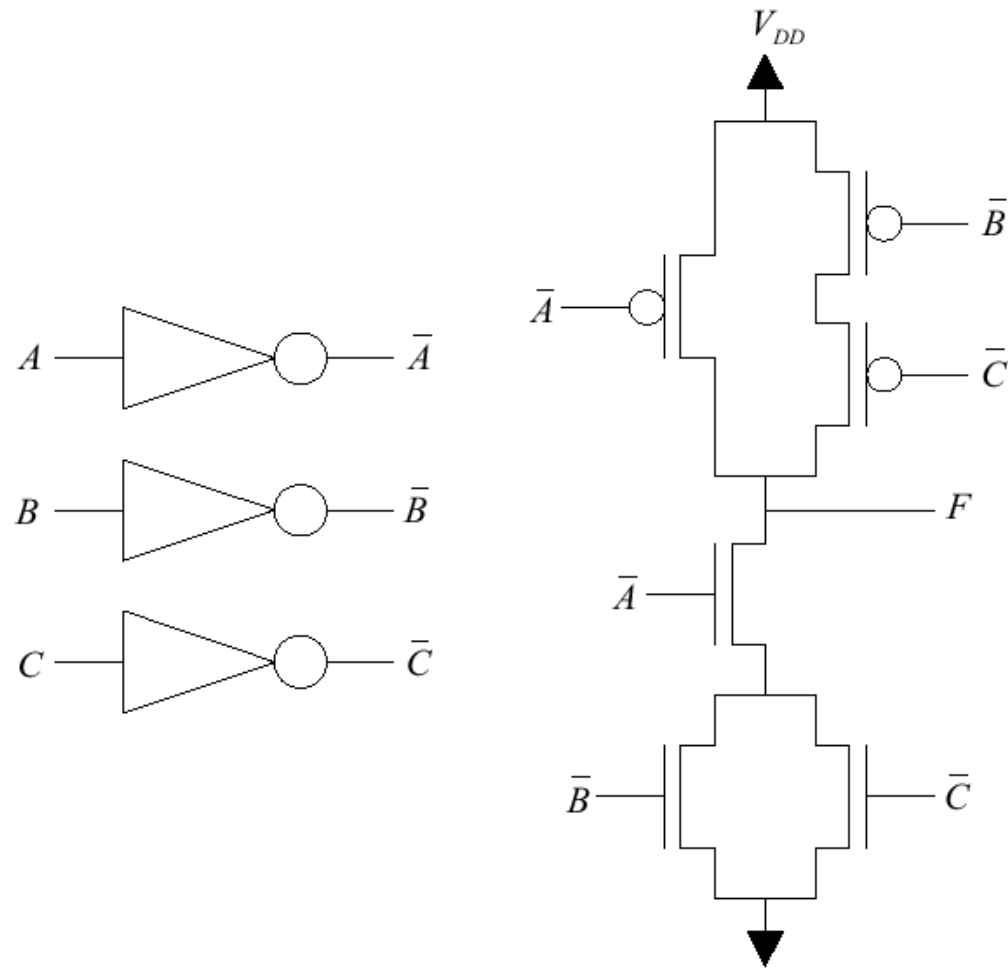


Fig. 2.37 Logic circuit designed for Example 2.4.

Example 2.4

 


Fig. 2.38 Minimized logic circuit for Example 2.4.

2-to-1 Multiplexer

 


Fig. 2.39 Symbol of a 2-to-1 multiplexer (MUX).

2-to-1 Multiplexer

S	i_0	i_1	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Fig. 2.40 Truth table of a 2-to-1 MUX.

2-to-1 Multiplexer

		$i_0 \ i_1$			
		00	01	11	10
S	0	0	0	1	1
	1	0	1	1	0

Fig. 2.41 Karnaugh map of a 2-to-1 MUX.

2-to-1 Multiplexer

 


Fig. 2.42 Complementary logic circuit for a 2-to-1 multiplexer.

2-to-1 Multiplexer

S	Z
0	i_0
1	i_1

Fig. 2.43 Modified truth table of a 2-to-1 multiplexer.

2-to-1 Multiplexer

 


Fig. 2.44 Pass-transistor logic for a 2-to-1 multiplexer.

Trickle Transistor



 


Fig. 2.45 Trickle transistor used to restore logic level.

T-Gate

 

Schematic

 

Symbol

Fig. 2.46 Transmission-gate (t-gate) structure and its symbol.

2-to-1 Multiplexer

 


Fig. 2.47 Transmission-gate logic for a 2-to-1 multiplexer.

4-to-1 Multiplexer

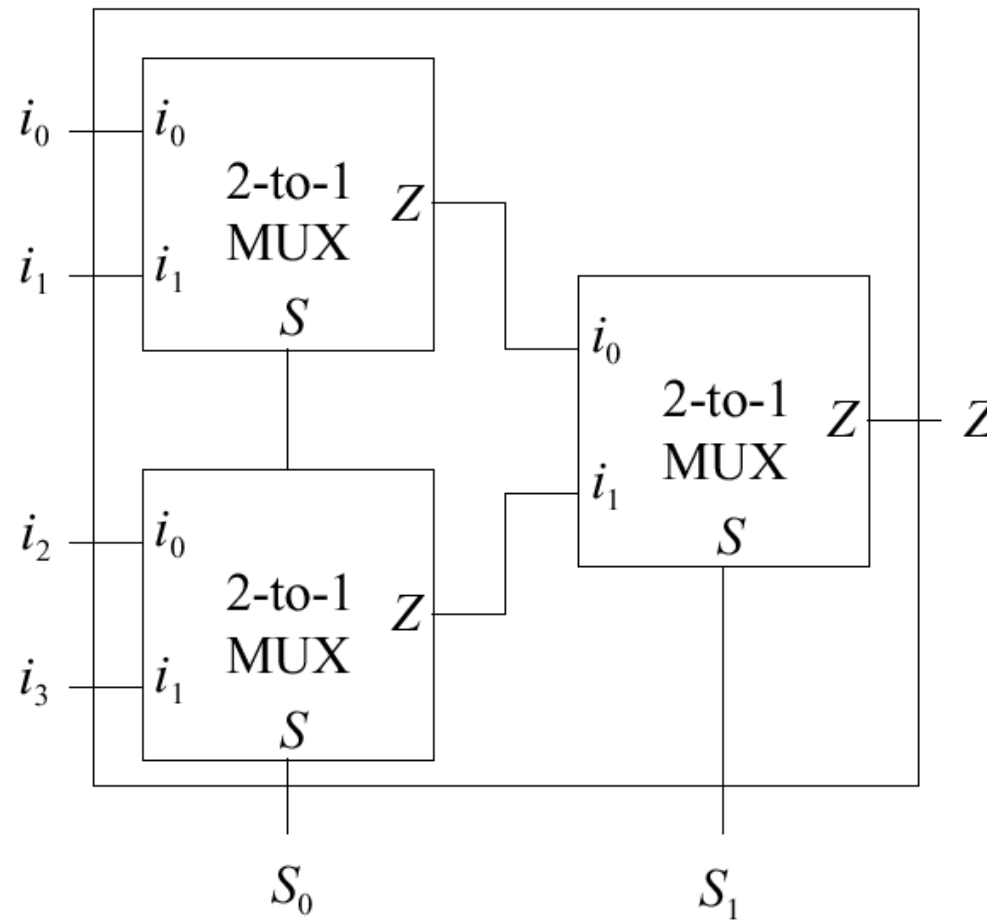


Fig. 2.48 4-to-1 multiplexer.

8-to-1 Multiplexer

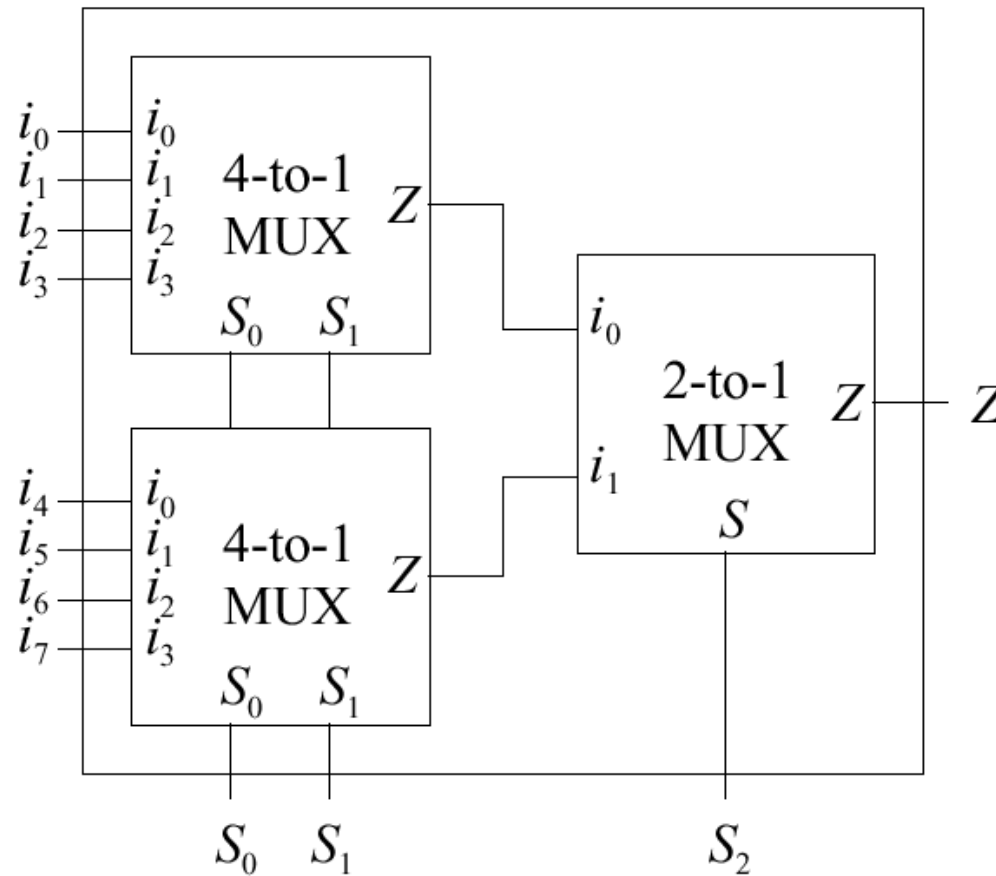


Fig. 2.49 8-to-1 multiplexer.

Hard-Wired Multiplexer

 


Fig. 2.50 Multiplexer hard-wired to implement $F = A + BC$.

Configurable Logic Block

 


Fig. 2.51 A multiplexer-based configurable logic block.

AND Gate

 


Fig. 2.52 Logic symbol of a two-input AND gate.

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

Fig. 2.53 Truth table of $F = AB$ in Example 1.5.

AND Gate

 


Fig. 2.54 2-to-1 multiplexer implementing a two-input AND gate.

Example 2.6

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Fig. 2.55 Truth table of $F = \overline{A}(B + \overline{C}) + A\overline{B}C$.

Example 2.6

A	B	F
0	0	\overline{C}
0	1	1
1	0	C
1	1	0

Fig. 2.56 Modified truth table of $F = \overline{A}(B + \overline{C}) + A\overline{B}C$ in Example 1.6.

Tri-State Inverter

 


Fig. 2.58 Tri-state inverter.