

---

# Chapter 12

## Array Processors

# Multiple Pipeline Structure

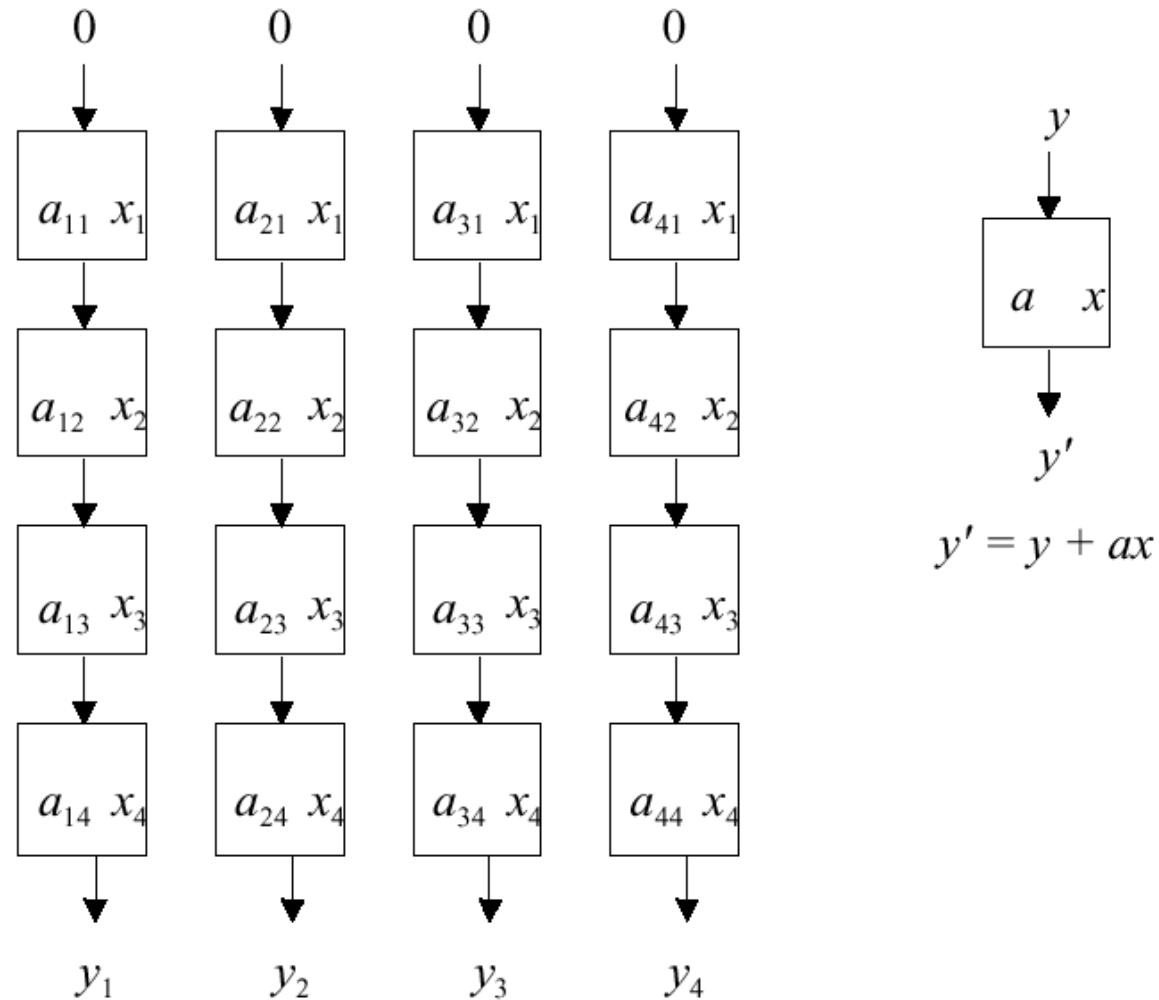


Fig. 12.1 Multiple pipeline structure for matrix-vector multiplication.

# Array Processor

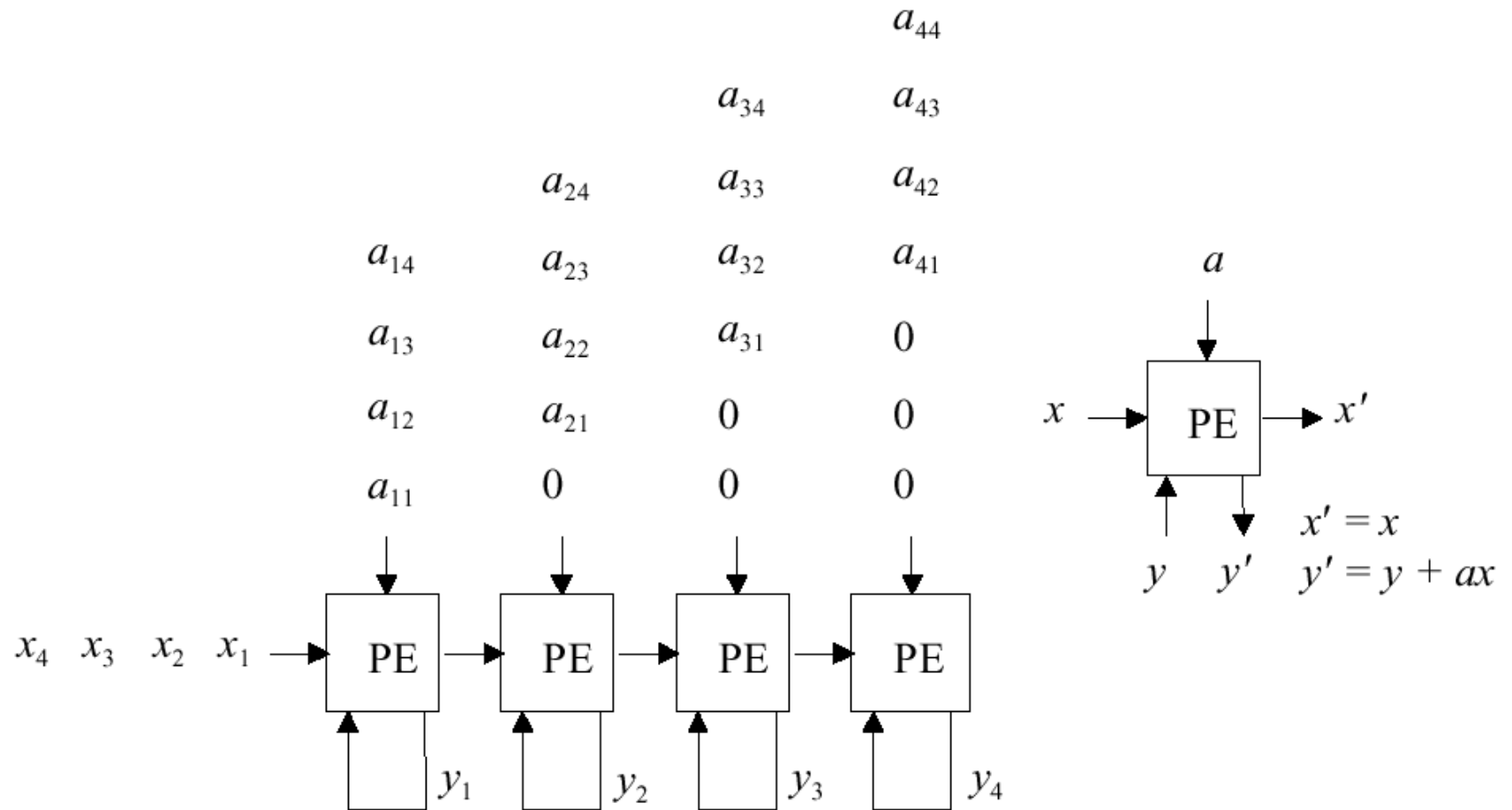


Fig. 12.2 Array processor for matrix-vector multiplication.

# Array Processor

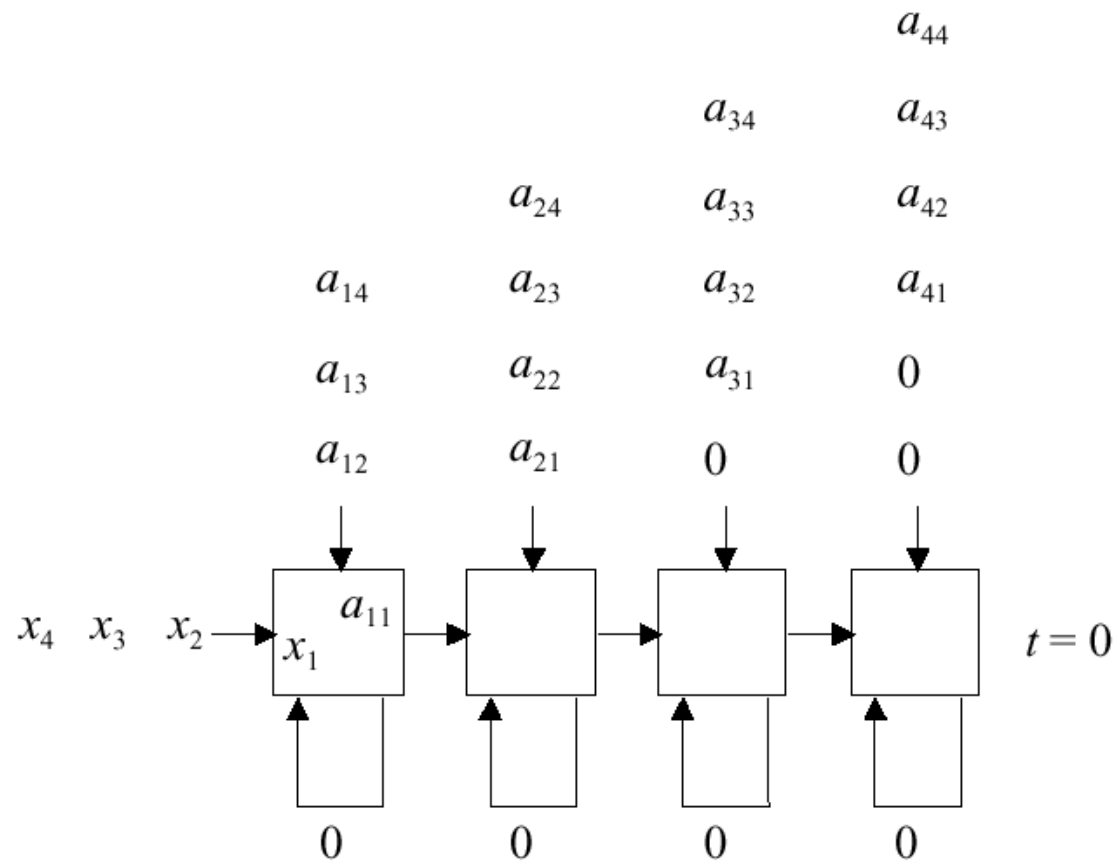


Fig. 12.3 Snapshot of the array processor at  $t = 0$ .

# Array Processor

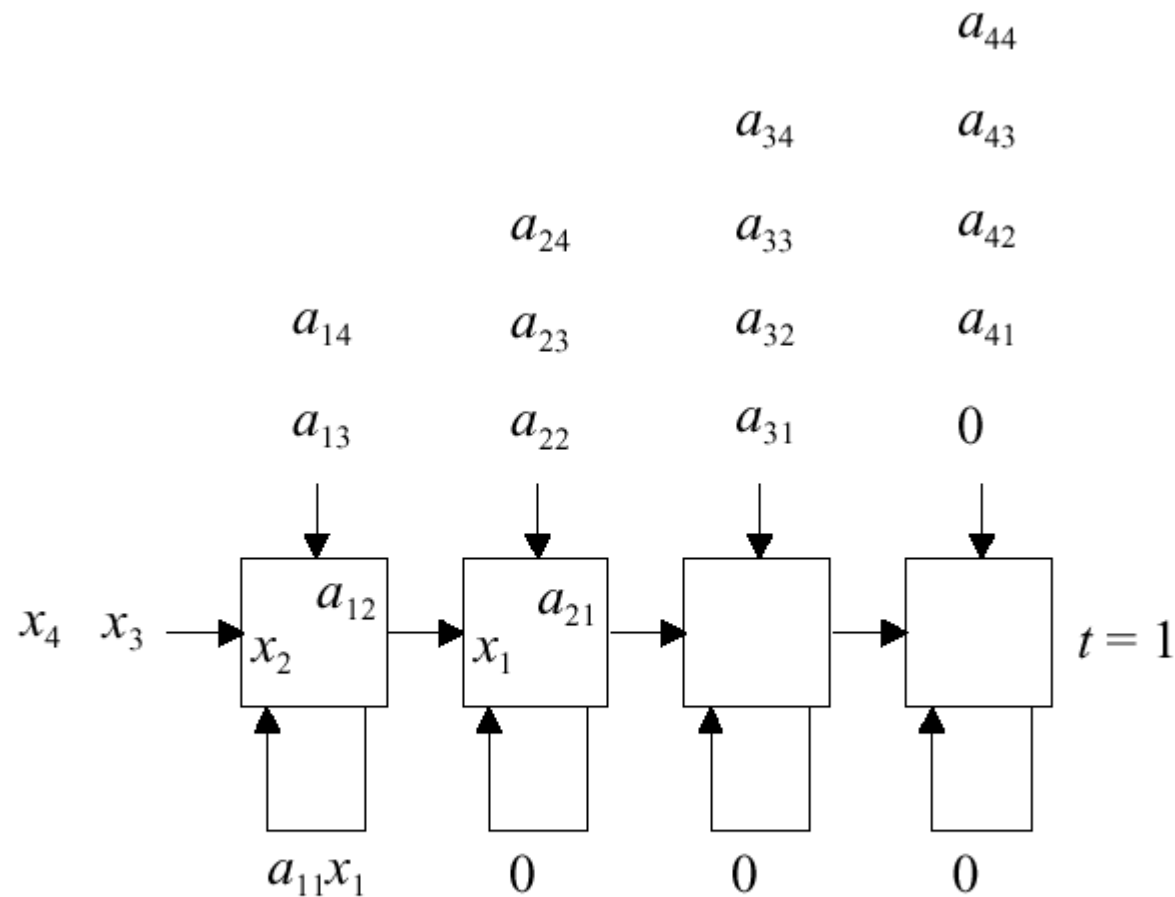


Fig. 12.4 Snapshot of the array processor at  $t = 1$ .

# Array Processor

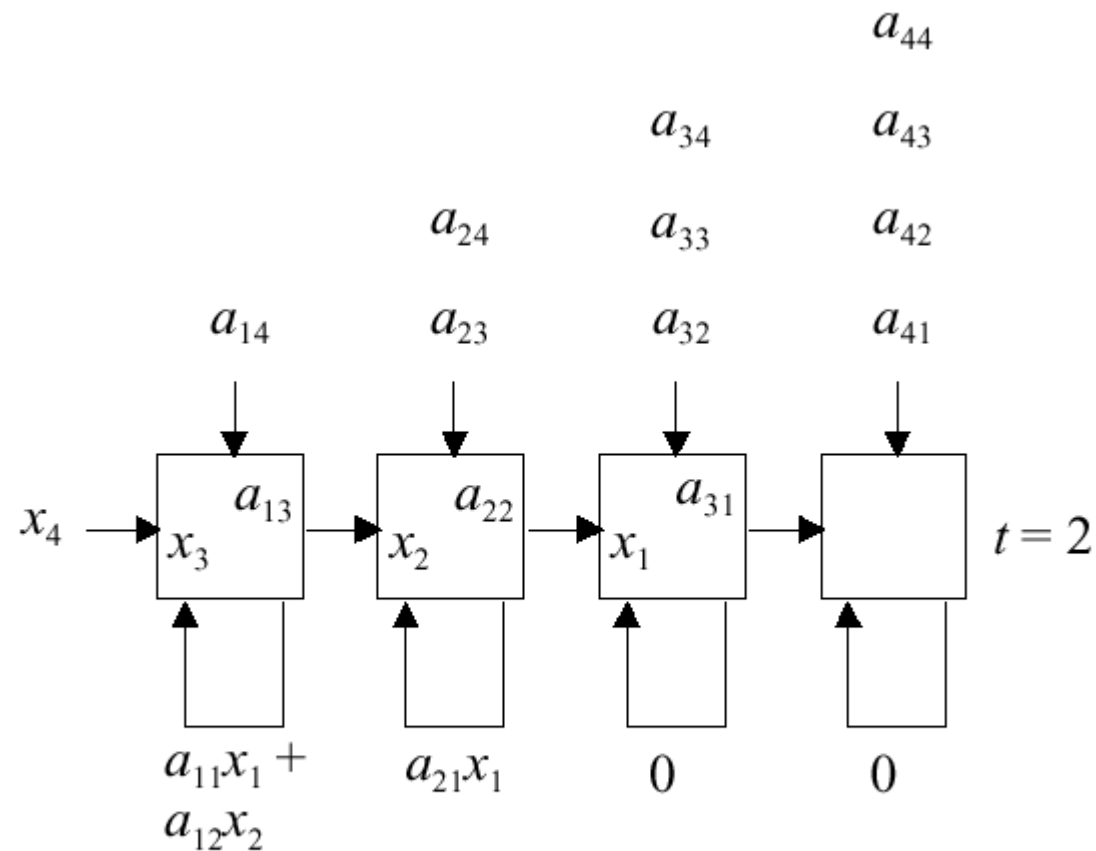


Fig. 12.5 Snapshot of the array processor at  $t = 2$ .

# Array Processor

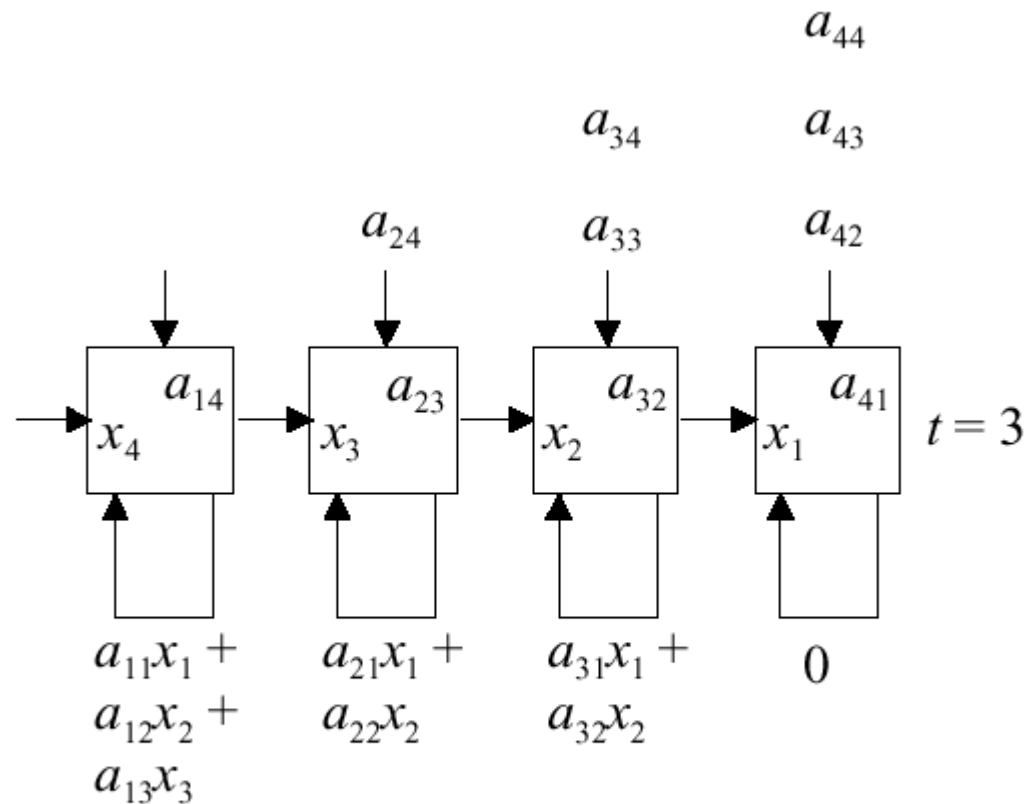


Fig. 12.6 Snapshot of the array processor at  $t = 3$ .

# Array Processor

 


Fig. 12.7 Snapshot of the array processor at  $t = 4$ .



# Linear Array Processor

 


Fig. 12.8 Linear array processor for matrix-vector multiplication.

# Array Processor

---

 


Fig. 12.9 Snapshots of the array processor shown in Fig. 12.8.

# Dependence Graph

 


Fig. 12.10 Dependence graph for matrix-vector multiplication.

# Dependence Graph

 


Fig. 12.11 Modified dependence graph with local interconnections.

# Projection

---

 


Fig. 12.12 Projection of a dependence graph to a signal flow graph.

# Direction Vectors

---

 


Fig. 12.13 Example vectors for direction representations.

# Projection Vector

 


Fig. 12.14 Valid projection vector and hyperplane set.

# Projections

 


Fig. 12.15 Three different projections of a dependence graph.



# Interconnection Mapping

---

 


Fig. 12.16 Mapping of interconnections.

# Interconnection Mapping

---

 


Fig. 12.17 Another interconnection mapping.

# Array Processor I/O

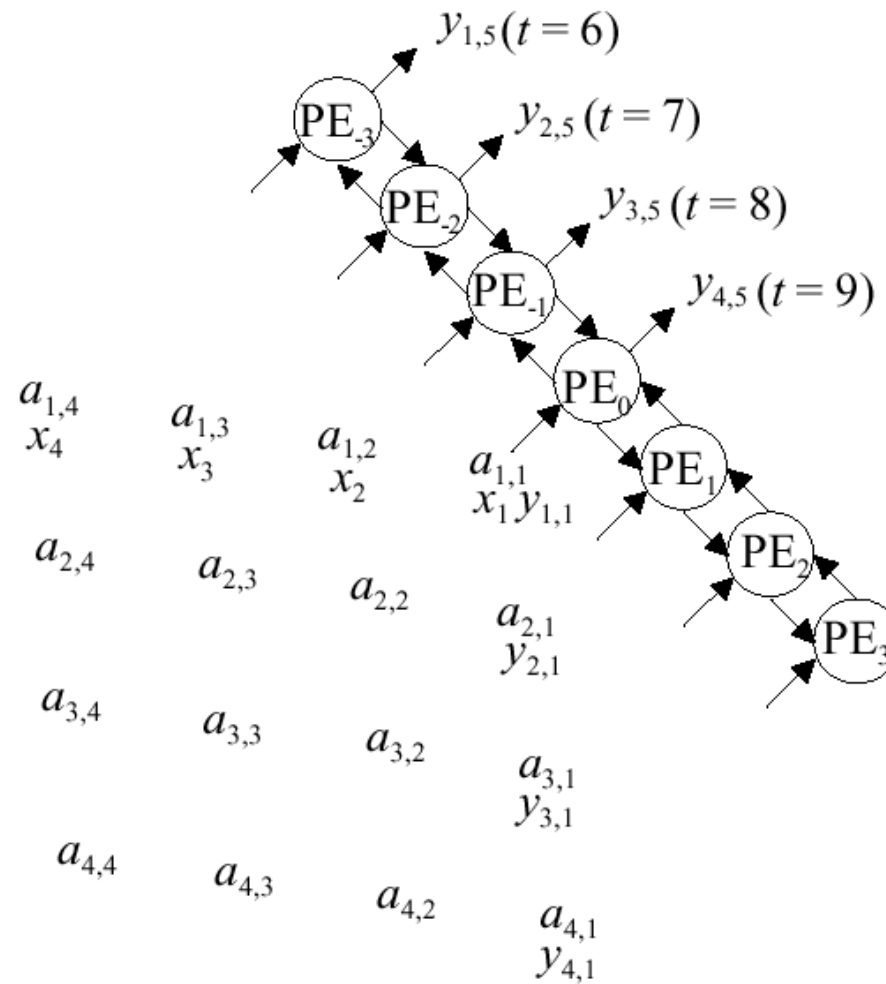


Fig. 12.18 I/O of the array processor.

# Wavefront Array PE

---

 


Fig. 12.19 PE used in a wavefront array: (a) a PE in activated state; and (b) a PE in waiting state.

# Wavefront Array PE

---

 


Fig. 12.20 Operations of a wavefront array PE.

# Wavefront Array Processor

---

 


Fig. 12.21 Deadlock wavefront array processor.

# Wavefront Array Processor

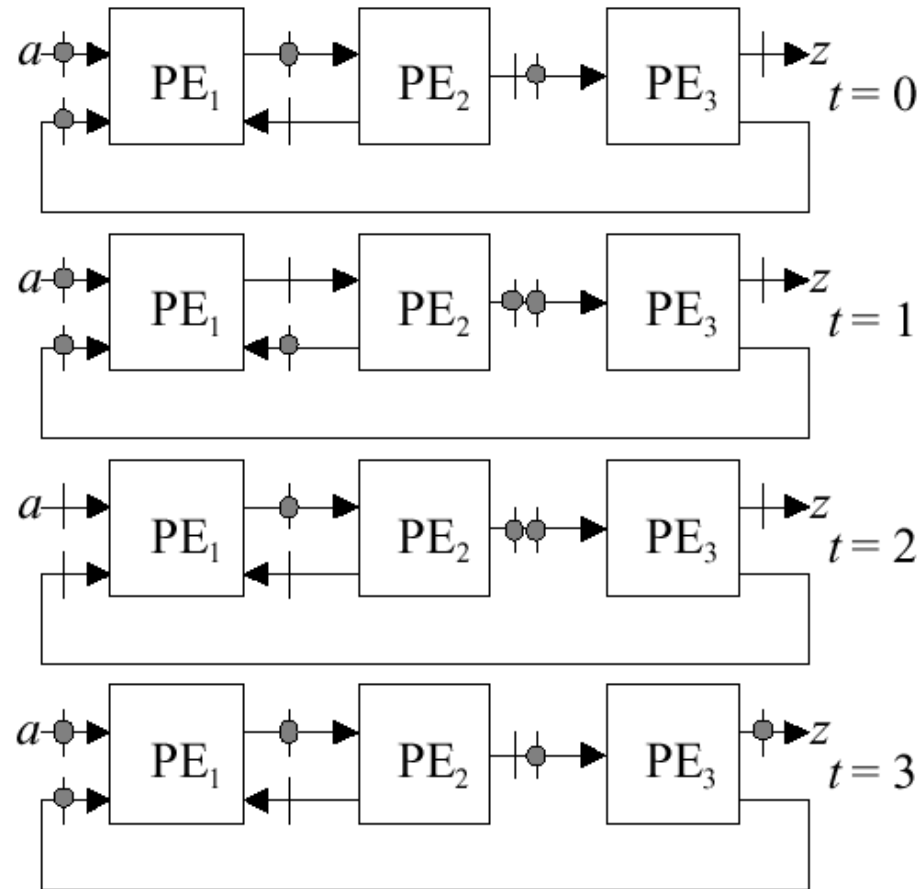


Fig. 12.22 Deadlock free wavefront array processor.

# Wavefront Array Processor

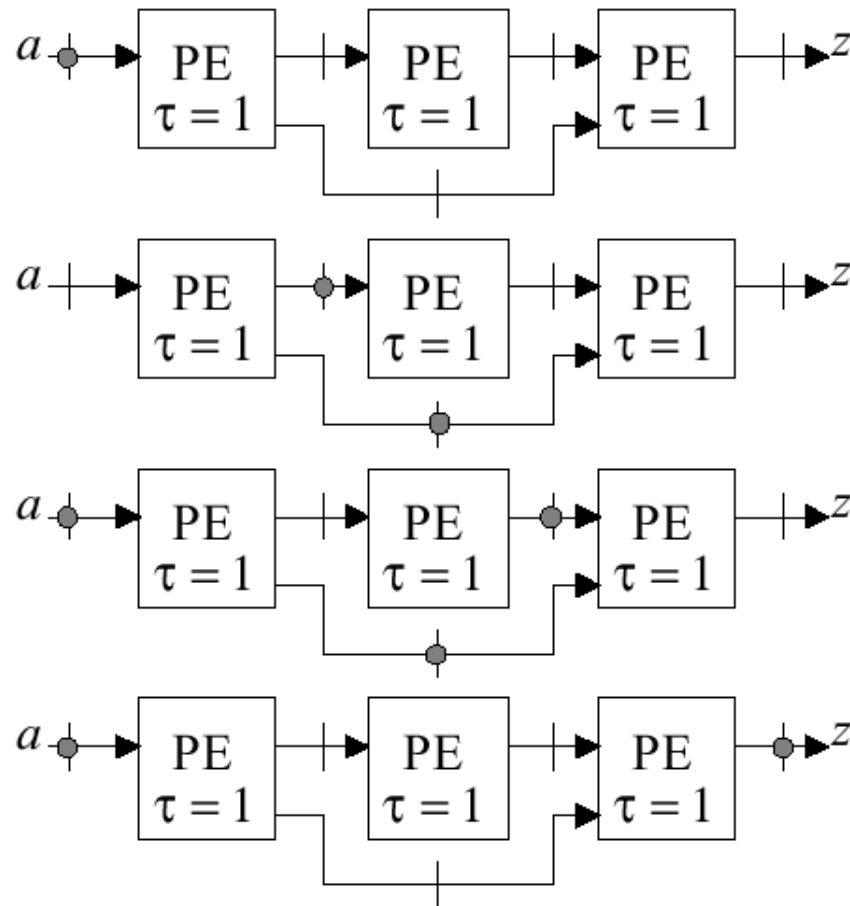


Fig. 12.23 Array processor with a throughput of  $1/3$ .



# Wavefront Array Processor

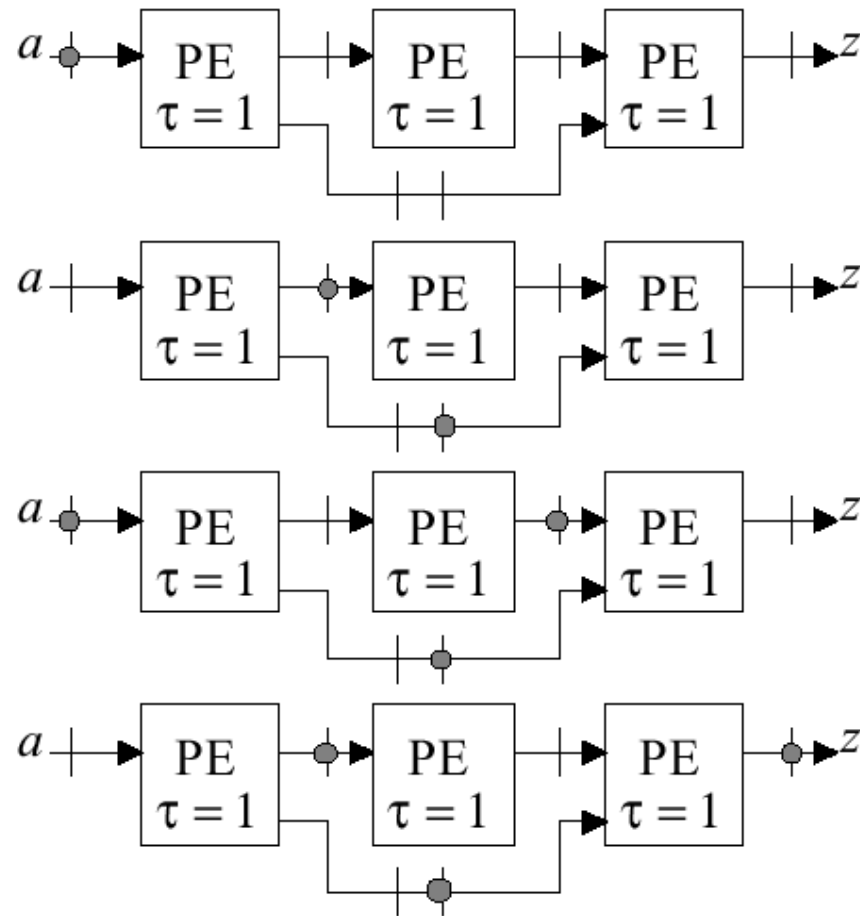


Fig. 12.24 Modified array processor with a throughput of 1/2.

# Wavefront Array Processor

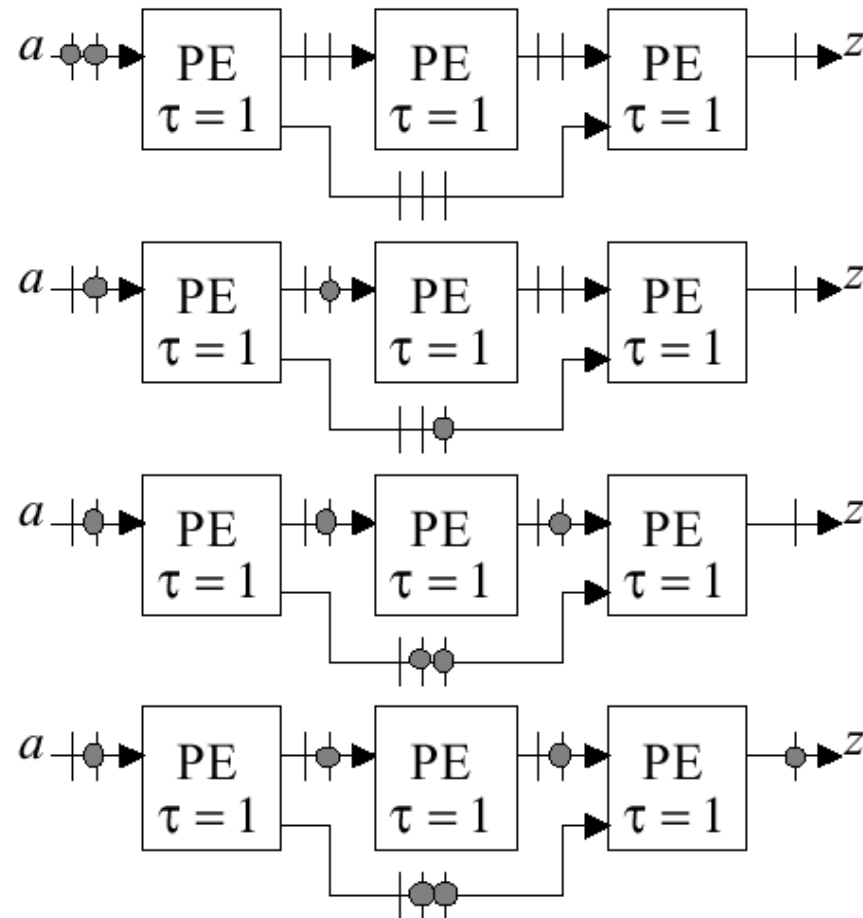


Fig. 12.25 Array processor with a throughput of 1.

# Directed Cycle

---

 


Fig. 12.26 Directed cycle in a wavefront array processor.

# Undirected Cycle

---

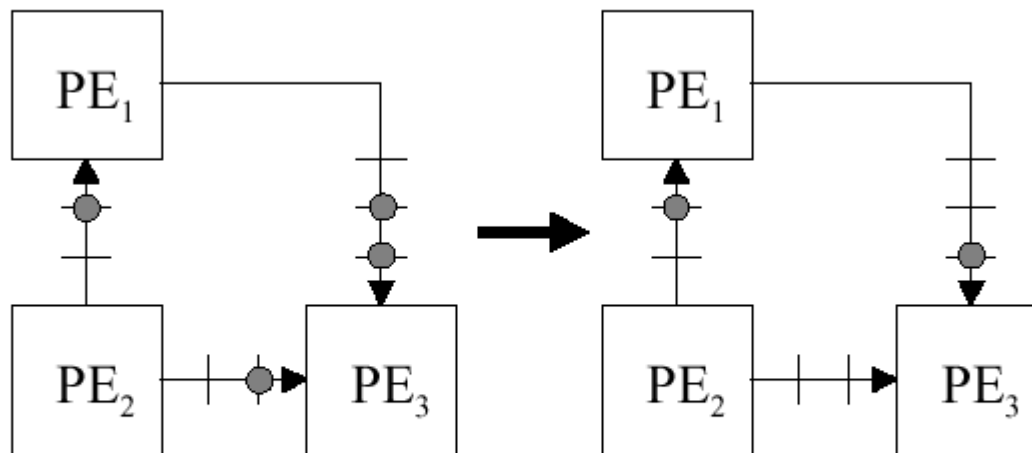


Fig. 12.27 An example demonstrating the undirected cycle property.

# Pipelining Period Analysis

---

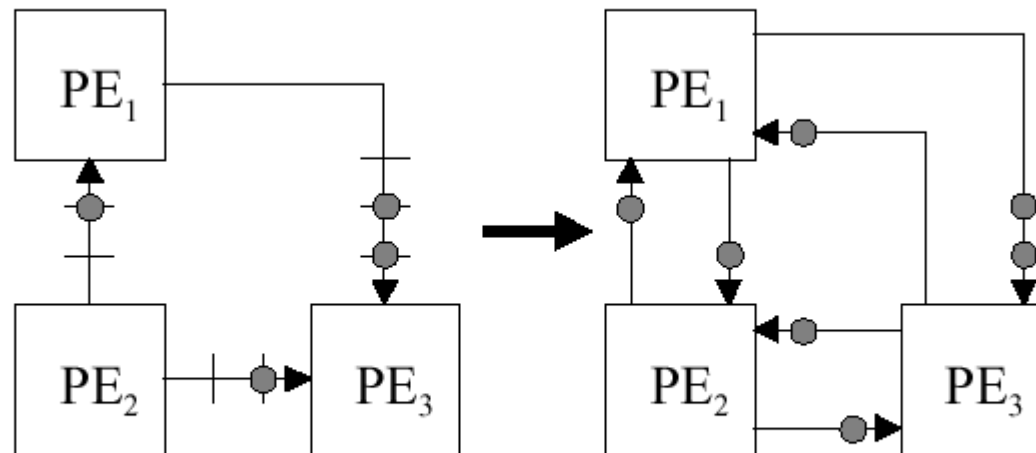


Fig. 12.28 Converting an array processor for pipelining period analysis.