
Chapter 6

Alternative Logic Structures

T-Gate Resistance

 


Fig. 6.1 Effective on-resistance of a t-gate.

Open-Drain Inverter

 


Fig. 6.2 An open-drain inverter.

Open-Drain Inverter

 


Fig. 6.3 Open drain inverter with a pull-up resistor.

Open-Drain Inverter

 


Fig. 6.4 Open-drain inverter driving another open-drain gate.

Pseudo-NMOS Inverter

 


Fig. 6.5 Pseudo-nMOS inverter.

Pseudo-NMOD NAND

 


Fig. 6.6 Transistor dimensions of pseudo-nMOS NAND gate.

Pseudo-NMOS NOR


 


Fig. 6.7 Transistor dimensions of pseudo-nMOS NOR gate.

 

PLA

 


Fig. 6.9 Block diagram of a PLA.

PLA

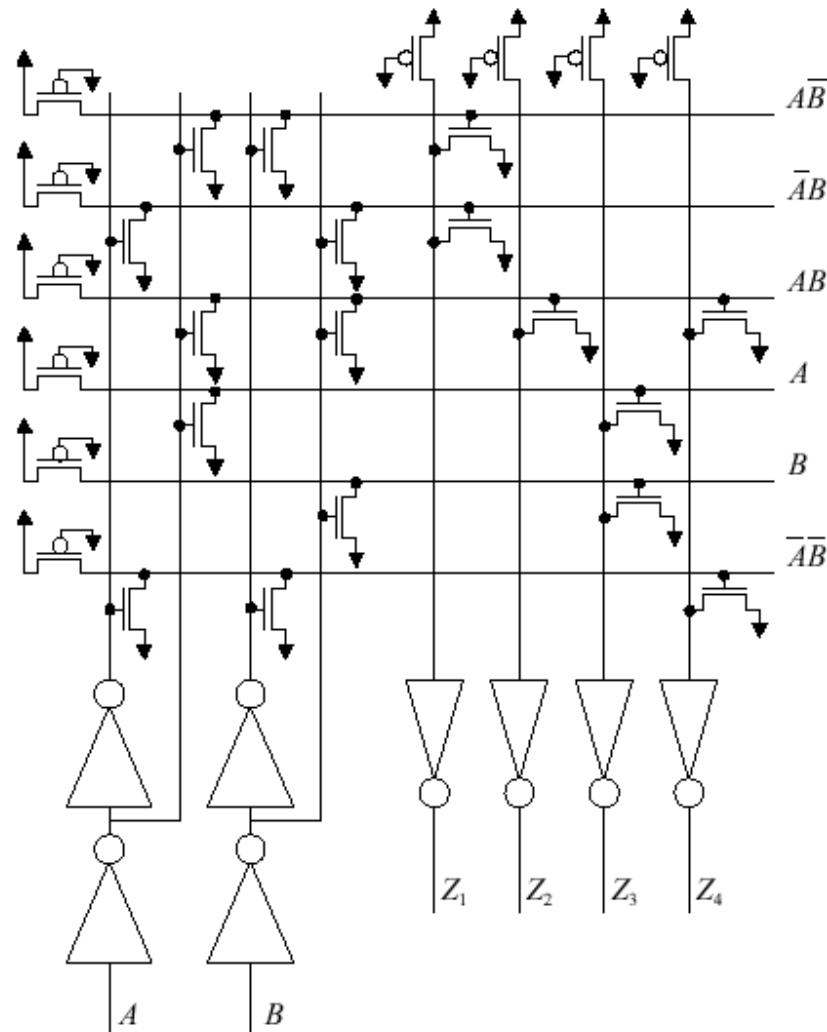


Fig. 6.10 PLA implementation of Example 6.1.

Dynamic CMOS

 


Fig. 6.11 Basic dynamic CMOS logic circuit structure.

Dynamic NAND Gate

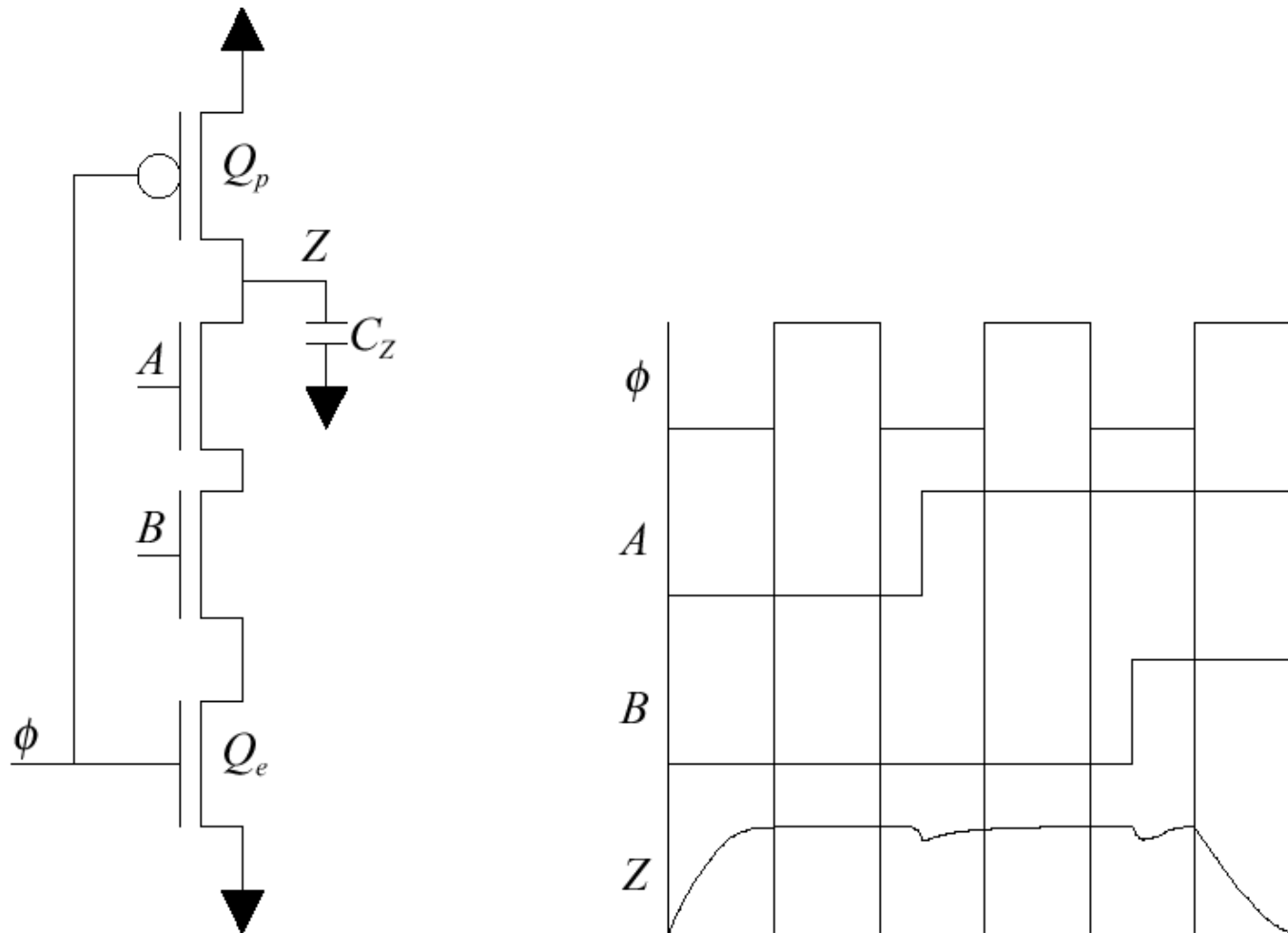


Fig. 6.12 Waveform diagram of a dynamic 2-input NAND gate.

Charge Sharing

 


Fig. 6.13 Circuit illustrating charge sharing.

Cascading Dynamic Inverters

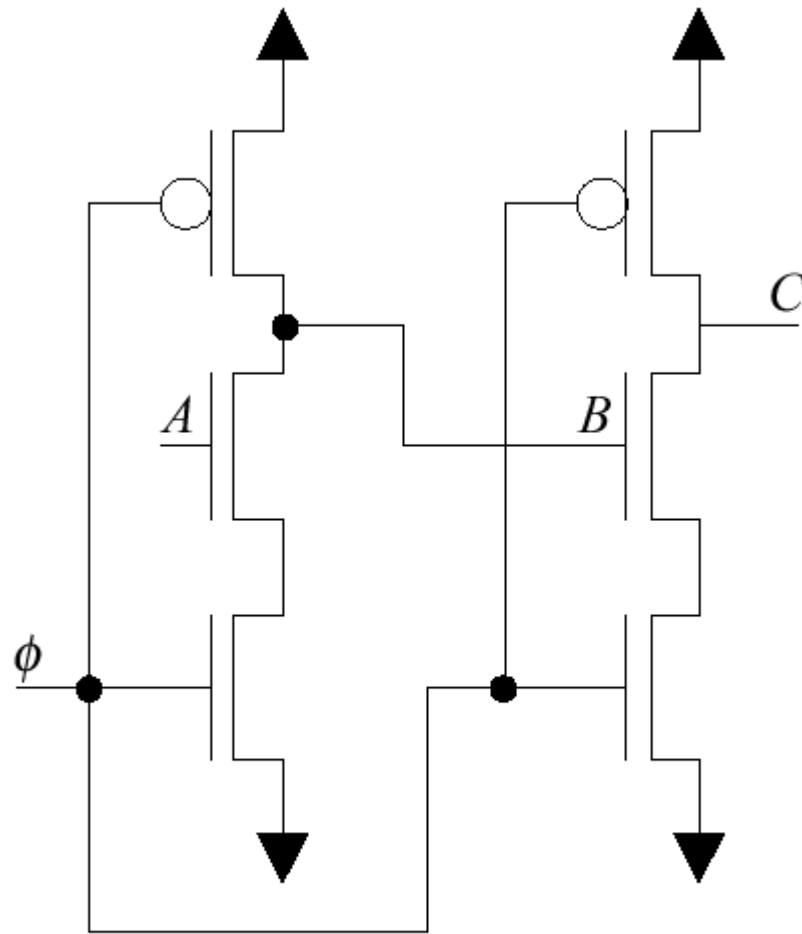


Fig. 6.14 Cascaded dynamic inverters.

Cascading Dynamic Inverters

 


Fig. 6.15 Waveform of two cascading dynamic inverters.

Non-Inverting Domino Logic

 


Fig. 6.16 Non-inverting domino logic circuit.

Inverting Domino Logic

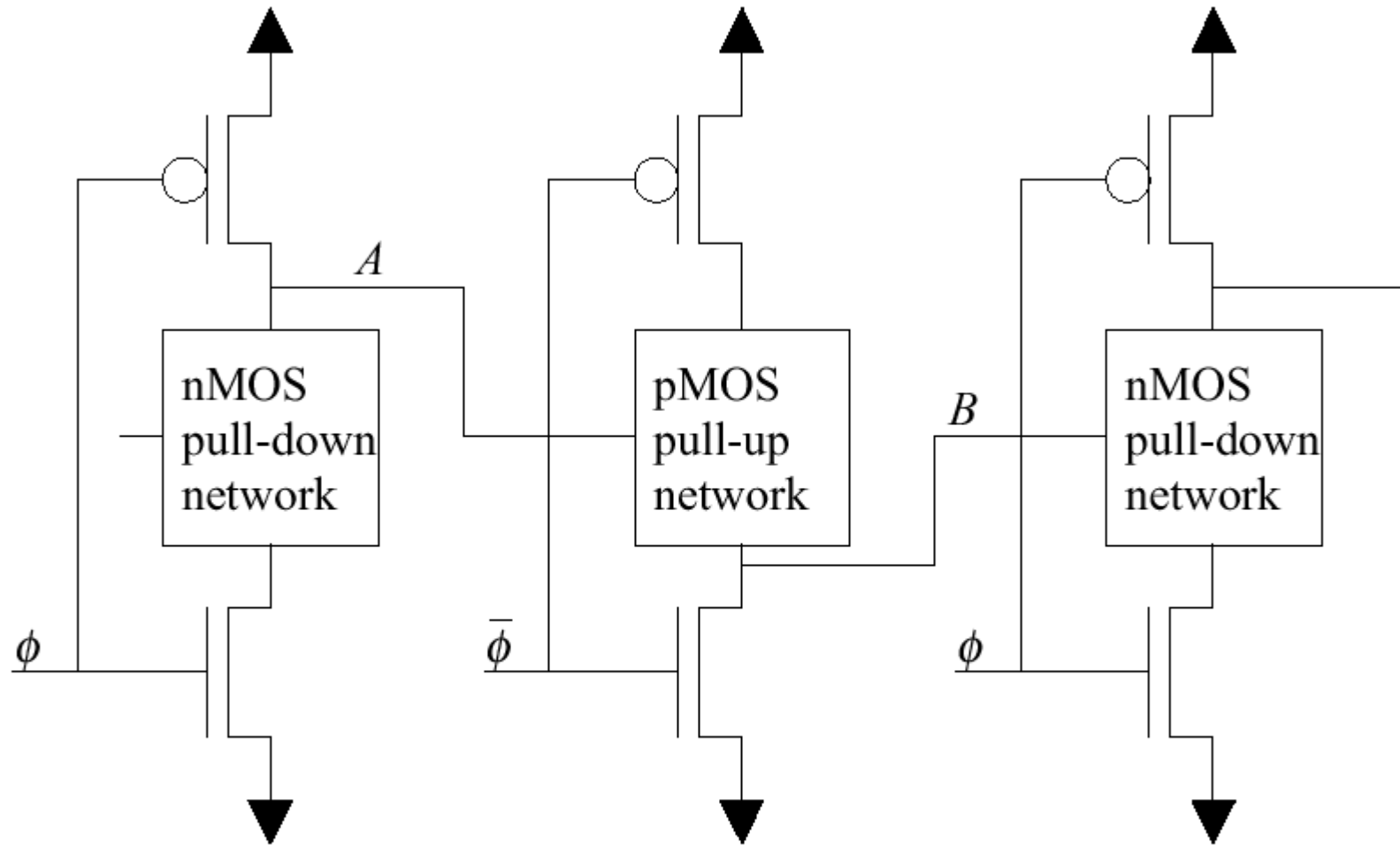


Fig. 6.17 Inverting domino logic circuits.

Dynamic Latch

 


Fig. 6.18 Dynamic D-latch.

Dynamic FF

 


Fig. 6.19 Negative edge triggered D-flip-flop.

BICMOS Inverter

 


Fig. 6.20 BiCMOS inverter.

BICMOD NAND Gate

 


Fig. 6.21 BiCMOS 2-input NAND gate.

Problem 6.6

 


Fig. 6.22 State diagram for problem 6.6.

Problem 6.11

 


Fig. 6.23 Circuit for Problem 6.11.

Problem 6.12

 


Fig. 6.24 Circuit diagram for Problem 6.12.