
Chapter 9

Testing

Fault Examples

Design errors	Incomplete specifications
	Incorrect logic implementations
	Incorrect wiring
	Design rule violations
	Excessive delays
	Glitches or hazards
	Slow rise/fall times
	Improper noise margins
	Improper timing margins
Fabrication errors	Shorts
	Opens
	Improper doping profiles
	Mask misalignments
	Incorrect transistor threshold voltages
Physical failures	Electron migration
	Cosmic radiation and α -particles

Fig. 9.1 Example faults found in integrated circuits.

NAND Gate

 


Fig. 9.2 CMOS NAND gate.

Example Circuit

 


Fig. 9.3 CMOS implementation of $Z = \overline{AB + CD}$.

NAND Gate Possible Faults

AB	Z (fault-free)	Z (A : s-a-1)	Z (A : s-a-0)	Z (Q_{nA} : s-op)	Z (Q_{nA} : bridged)
00	1	1	1	1	1
01	1	0	1	1	X
10	1	1	1	1	1
11	0	0	1	HiZ	0

Fig. 9.4 A few possible faults in a CMOS NAND gate.

D-Algorithm

AND	0	1	D	\bar{D}	X
0	0	0	0	0	0
1	0	1	D	\bar{D}	X
D	0	D	D	0	X
\bar{D}	0	\bar{D}	0	\bar{D}	X
X	0	X	X	X	X

OR	0	1	D	\bar{D}	X
0	0	1	D	\bar{D}	X
1	1	1	1	1	1
D	D	1	D	1	X
\bar{D}	\bar{D}	1	1	\bar{D}	X
X	X	1	X	X	X

Fig. 9.5 5-valued logic operations in D-algorithm.

NAND Gate

 


Fig. 9.6 2-input NAND gate.

NAND Truth Table

a	b	$c: \text{s-a-0}$
X	X	0

Fig. 9.7 Truth table of a NAND gate with its output s-a-0.

NAND Gate Singular Cover

a	b	\overline{ab}
0	X	1
X	0	1
1	1	0

Fig. 9.8 Singular cover for two-input NAND gate.

Intersecting Rules

Intersect (\wedge)	0	1	X
0	0	\bar{D}	0
1	D	1	1
X	0	1	X

Fig. 9.9 Intersecting rules.

NOR Gate Singular Cover

 


Fig. 9.10 Two-input NOR gate.

a	b	c
0	X	1
1	X	0

Fig. 9.11 Singular cover for NOR gate with b : s-a-0.

NOR Gate Singular Cover

a	b	c
0	0	1
1	X	0
X	1	0

Fig. 9.12 Singular cover for fault-free NOR gate.

D-Algorithm

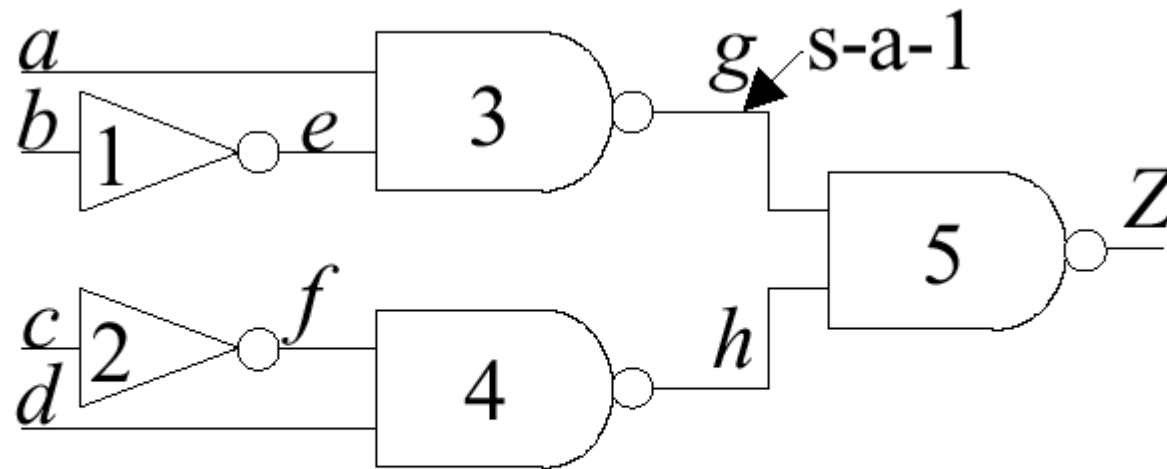


Fig. 9.13 Example circuit for D-algorithm.

D-Algorithm

	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>	<i>h</i>	<i>Z</i>
Primitive D-cube (gate 3)	1				1		<i>D</i>		
Propagation D-cube (gate 5)							<i>D</i>	1	\bar{D}
Singular cover (gate 1)		0			1				
Singular cover (gate 4)				<i>X</i>		0		1	
Singular cover (gate 2)			1			0			

Fig. 9.14 D-algorithm.

Bridging

 


Fig. 9.15 Bridging fault model.

Full Adder

 


Fig. 9.16 Full adder.

Test Patterns

Fault	Test Patterns (<i>abc</i>)	Fault-free output (<i>de</i>)	Faulty output (<i>de</i>)
<i>a</i> : s-a-1	000	00	01
	001	01	10
	010	01	10
	011	10	11
<i>b</i> : s-a-1	000	00	01
	001	01	10
	100	01	10
	101	10	11
<i>c</i> : s-a-1	000	00	01
	010	01	10
	100	01	10
	110	10	11
<i>a</i> : s-a-0	111	11	10
	100	01	00
	101	10	01
	110	10	01
<i>b</i> : s-a-0	111	11	10
	010	01	00
	011	10	01
	110	10	01
<i>c</i> : s-a-0	111	11	10
	001	01	00
	011	10	01
	101	10	01
<i>d</i> : s-a-1	000	00	10
	001	01	11
	010	01	11
	100	01	11
<i>e</i> : s-a-1	110	10	11
	000	00	01
<i>d</i> : s-a-0	011	10	00
	101	10	00
	110	10	00
	111	11	01
<i>e</i> : s-a-0	001	01	00
	010	01	00
	100	01	00
	111	11	10

Fig. 9.17 Test patterns for all stuck-at faults in a full adder.

Fault Matrix

Test vector	a s-a-1	b s-a-1	c s-a-1	a s-a-0	b s-a-0	c s-a-0	d s-a-1	e s-a-1	d s-a-0	e s-a-0
000	1	1	1				1	1		
001	1	1				1		1	1	
010	1		1		1			1	1	
011	1				1	1				
100		1	1	1				1	1	
101		1		1		1				1
110			1	1	1		1			1
111				1	1	1			1	1

Fig. 9.18 Fault matrix.

Full Adder Implementation

 


Fig. 9.19 A gate level implementation of a full adder.

Sequential Circuit Testing

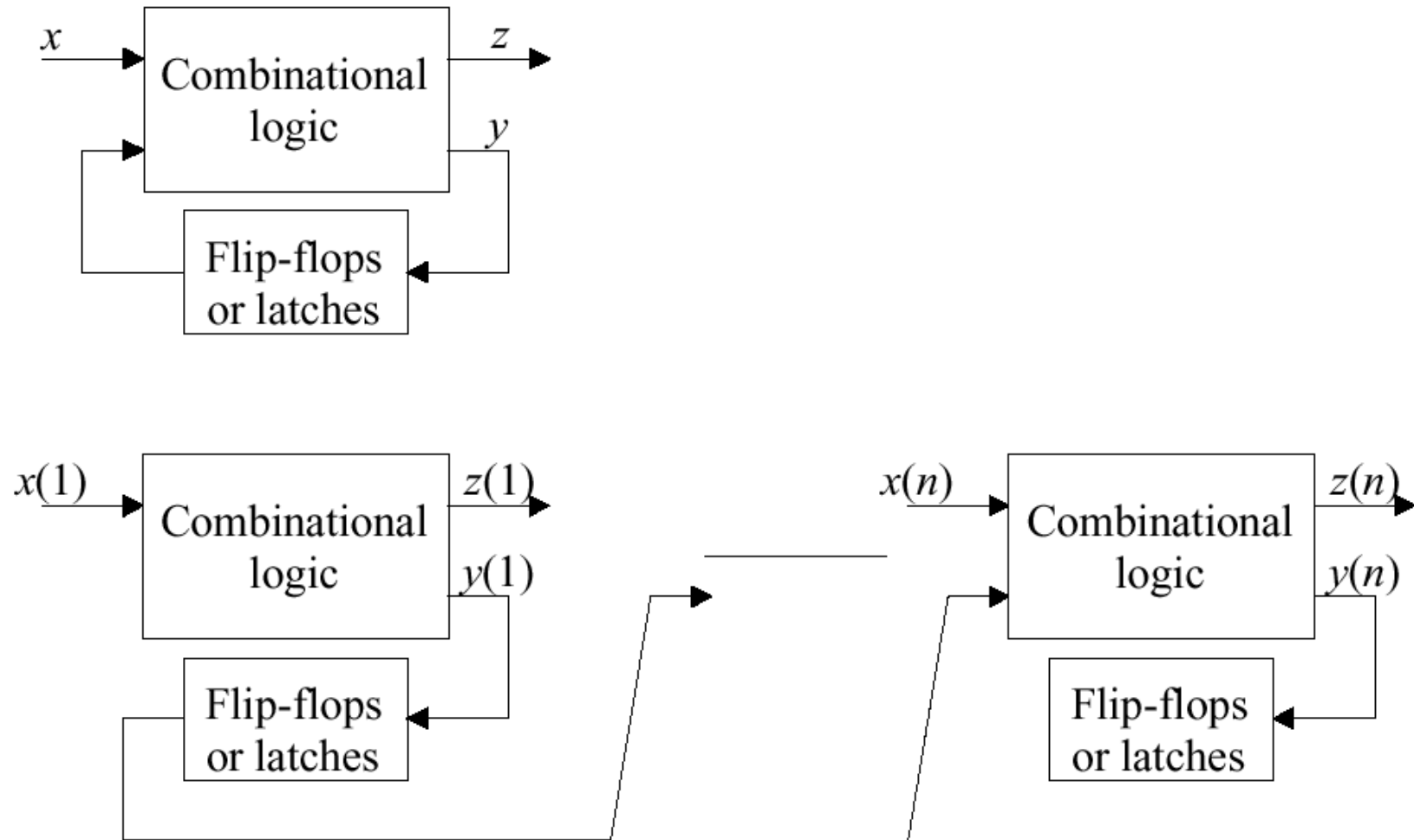


Fig. 9.20 Sequential circuit modeled as combinational circuit for test generation.

Shift Register with Feedback

 


Fig. 9.21 Shift register with feedback.

Linear Feedback Shift Register

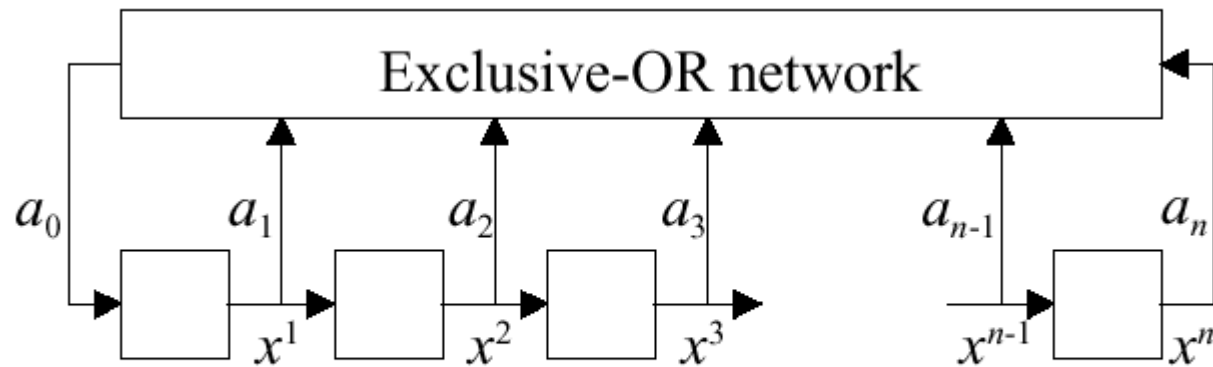


Fig. 9.22 Linear feedback shift register.

Pseudo-Random Pattern Generator

 


Fig. 9.23 Linear feedback shift register as a pseudo-random pattern generator.

Signature Analyzer

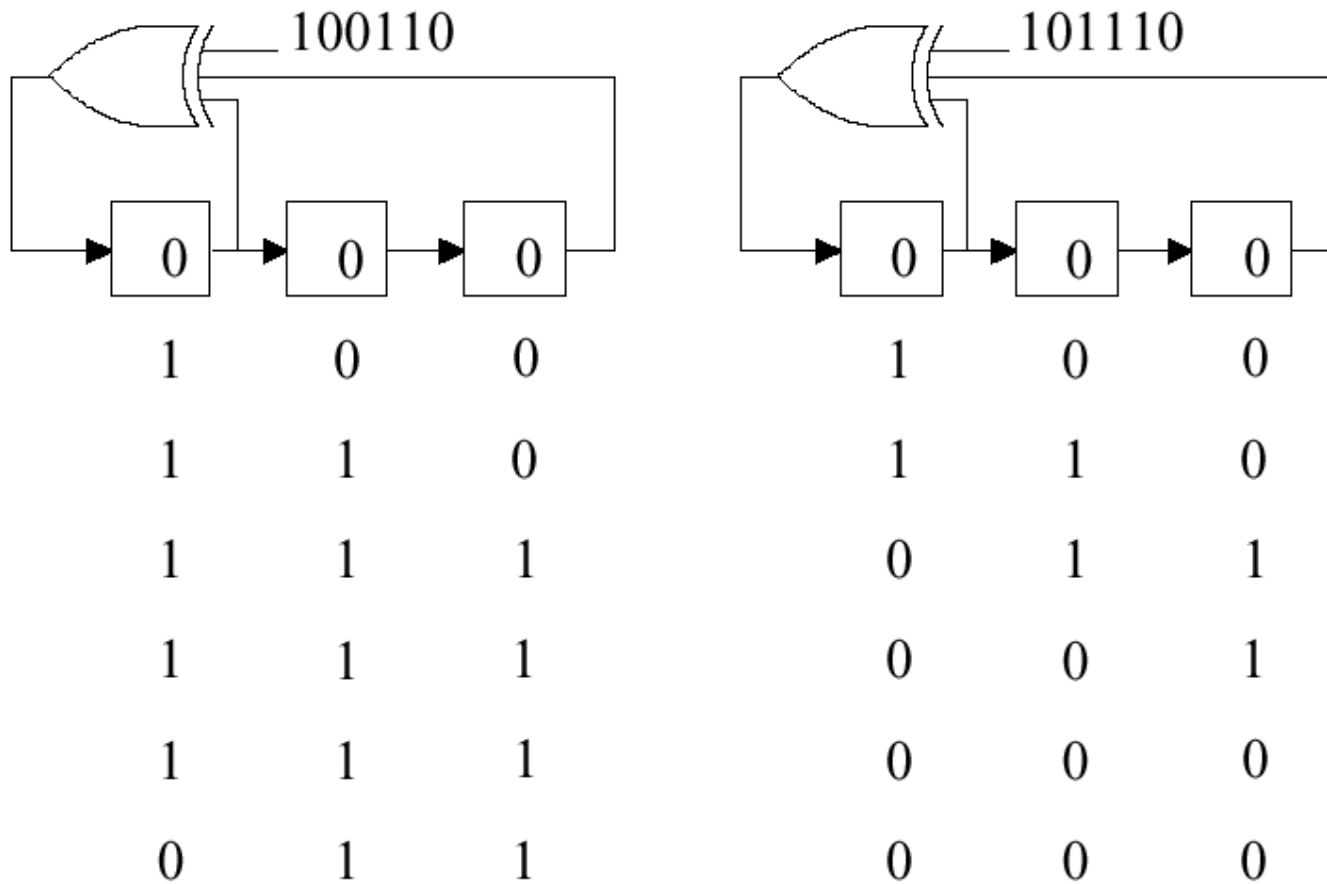


Fig. 9.24 Signature analyzer.

Test Setup

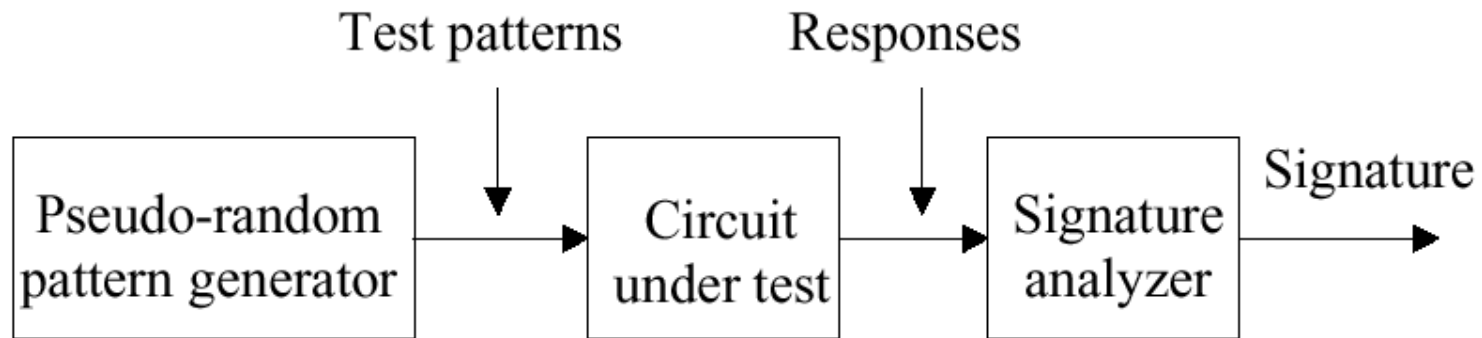


Fig. 9.25 Setup of a pseudo-random pattern generator and a signature analyzer to test a circuit.

Problem 9.3

 


Fig. 9.26 Circuit for Problem 9.3.