
Chapter 4

CMOS Circuit Characterization

NMOS Characteristics

 


Fig. 4.1 Setup for measuring the i_D - v_{DS} characteristics of an nMOS transistor.

NMOS Characteristics

 


Fig. 4.2 The i_D - v_{DS} characteristics for the nMOS transistor.

PMOS Characteristics

 


Fig. 4.3 Setup for measuring the i_D - v_{DS} characteristics of a pMOS transistor.

Operation Regions

Operating Regions	nMOS ($v_{GS} > 0, v_{DS} > 0, V_{tn} > 0$)	pMOS ($v_{GS} < 0, v_{DS} < 0, V_{tp} < 0$)
Cutoff	$v_{GS} \leq V_{tn}, i_D = 0$	$v_{GS} \geq V_{tp}, i_D = 0$
Linear	$v_{GS} > V_{tn}$ $v_{DS} < v_{GS} - V_{tn}$ $i_D =$ $k_n \frac{W}{L} \left[(v_{GS} - V_{tn})v_{DS} - \frac{1}{2}v_{DS}^2 \right]$	$v_{GS} < V_{tp}$ $v_{DS} > v_{GS} - V_{tp}$ $i_D =$ $k_p \frac{W}{L} \left[(v_{GS} - V_{tp})v_{DS} - \frac{1}{2}v_{DS}^2 \right]$
Saturation	$v_{GS} > V_{tn}$ $v_{DS} > v_{GS} - V_{tn}$ $i_D = \frac{1}{2}k_n \frac{W}{L} (v_{GS} - V_{tn})^2$	$v_{GS} < V_{tp}$ $v_{DS} < v_{GS} - V_{tp}$ $i_D = \frac{1}{2}k_p \frac{W}{L} (v_{GS} - V_{tp})^2$

Fig. 4.4 Operation regions of nMOS and pMOS transistors.

Inverter Voltage Transfer

 


Fig. 4.5 CMOS inverter and its voltage transfer characteristic.

Operation Regions

 


Fig. 4.6 Relationship between the nMOS and pMOS transistors in an inverter.

Spice Model

```
.MODEL nfet NMOS LEVEL=2 LD=0.12U TOX=200E-10
+NSUB=1.0E+16 VTO=0.8 KP=5.0E-5 GAMMA=0.45 PHI=0.6
+UO=700 VMAX=70000 XJ=0.6U LAMBDA=.02 NSS=0.0
+TPG=1.00 RSH=0 CGSO=0.9E-10 CGDO=0.9E-10 CJ=1.4E-4
+MJ=0.6 CJSW=6.5E-10 MJSW=0.3
```

```
.MODEL pfet PMOS LEVEL=2 LD=0.18U TOX=200E-10
+NSUB=1.5E+15 VTO=-0.7 KP=2.0E-5 GAMMA=0.45 PHI=0.6
+UO=250 VMAX=34600 XJ=0.4U LAMBDA=.04 NSS=0.0
+TPG=-1.00 RSH=0 CGSO=1.4E-10 CGDO=1.4E-10 CJ=2.4E-4
+MJ=0.5 CJSW=3.5E-10 MJSW=0.3
```


Spice Deck

* SPICE DECK created for a CMOS inverter Z=not(A)

```
M1 1 2 3 1 pfet L=1.0U W=4.0U
M2 3 2 0 0 nfet L=1.0U W=4.0U
C3 3 0 0.028000PF
```

```
* A      2
* GND    0
* VDD    1
* Z      3
```

* CMOS SPICE model parameters

```
.MODEL nfet NMOS LEVEL=2 LD=0.12U TOX=200E-10
+NSUB=1.0E+16 VTO=0.8 KP=5.0E-5 GAMMA=0.45 PHI=0.6
+UO=700 VMAX=70000 XJ=0.6U LAMBDA=.02 NSS=0.0
+TPG=1.00 RSH=0 CGSO=0.9E-10 CGDO=0.9E-10 CJ=1.4E-4
+MJ=0.6 CJSW=6.5E-10 MJSW=0.3
```

Spice Deck

```
.MODEL pfet PMOS LEVEL=2 LD=0.18U TOX=200E-10
+NSUB=1.5E+15 VTO=-0.7 KP=2.0E-5 GAMMA=0.45 PHI=0.6
+UO=250 VMAX=34600 XJ=0.4U LAMBDA=.04 NSS=0.0
+TPG=-1.00 RSH=0 CGSO=1.4E-10 CGDO=1.4E-10 CJ=2.4E-4
+MJ=0.5 CJSW=3.5E-10 MJSW=0.3
```

```
* Power source
vps 1 0 dc 5
```

```
* Input waveform
vA 2 0 dc 0 pwl(0ns 0 0.01ns 5 10ns 5
+10.01ns 0 20ns 0 20.01ns 5 30ns 5)
```

```
* Perform a transient analysis with a step size
* of .1 ns for the duration of 40 ns.
.tran 0.1ns 40ns
```

```
* Provide values and plots for V(A) and V(Z)
.print tran v(2) v(3)
.plot tran v(2) v(3)

.end
```

Spice Simulation

 


Fig. 4.7 Inverter circuit for SPICE simulation.

Spice Simulation

 


Fig. 4.8 SPICE simulation result of an inverter.

Resistive Switch Model

 


Fig. 4.9 Resistive switch model of an nMOS transistor.

Dynamic Behavior

 


Fig. 4.10 Dynamic behavior of an nMOS transistor being turned on.

Propagation Delay

 


Fig. 4.11 Definition of propagation delay.

RC Timing Model

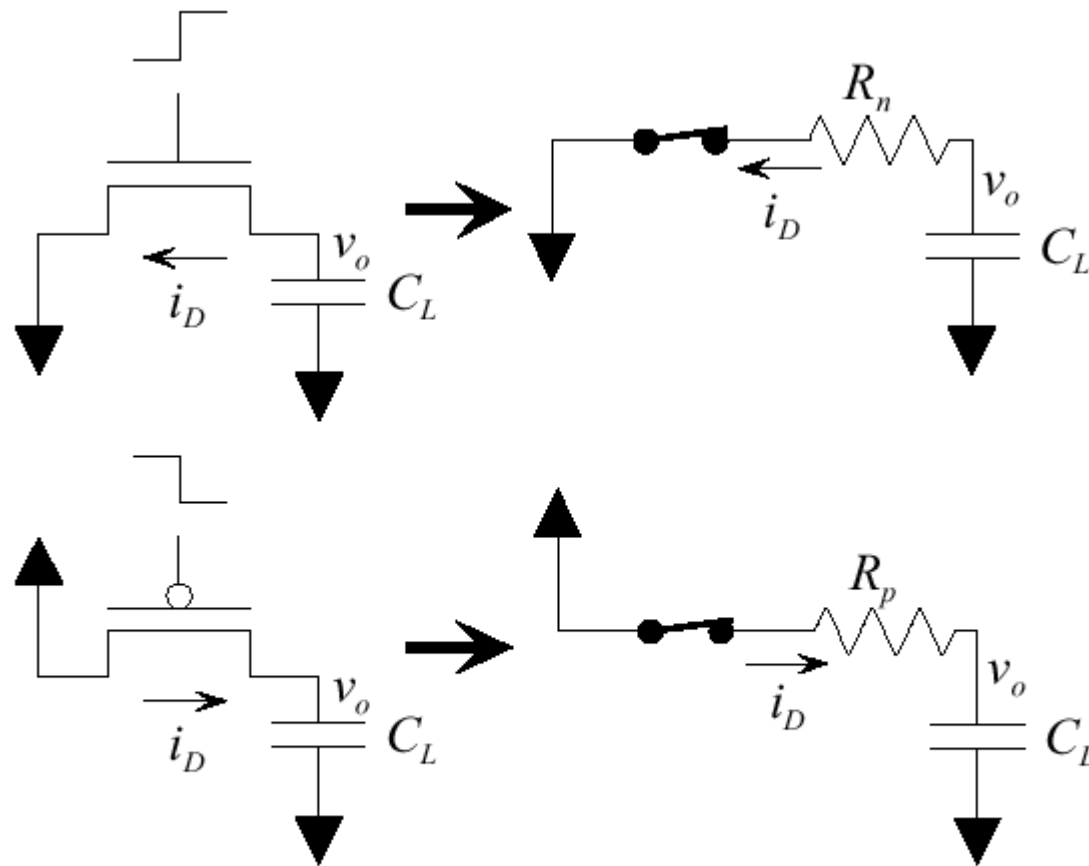


Fig. 4.12 RC timing models.

Resistance

 


Fig. 4.13 Determination of resistance value.

Example Resistance and Capacitance

Layer	Ω/square
Metal 1 and 2	0.05
n-type Diffusion	2
p-type Diffusion	2
Polysilicon	4
nMOS Channel (effective)	6 K
pMOS Channel (effective)	15 K
Capacitance	fF/μm^2
nMOS and pMOS gate	1
Diffusion (area)	0.8
Diffusion (periphery)	0.3 (fF/ μm)
Polysilicon	0.1
Metal 1	0.05
Metal 2	0.02

Fig. 4.14 Example resistance and capacitance values.

Resistance

 


Fig. 4.15 Resistance value calculation of a polysilicon wire.

Capacitance

 


Fig. 4.16 Determination of capacitance value.

Diffusion Capacitance

 


Fig. 4.17 Diffusion capacitance.

Resistance and Capacitance

 


Fig. 4.18 Resistance and capacitance value estimation.

Wire Capacitance

 


Fig. 4.19 Capacitance between two wires: (a) Before sub-micron;
(b) Deep sub-micron.

RC Tree

 


Fig. 4.20 RC tree.

Load

 


Fig. 4.21 Two-input NAND gate driving an inverter.

RC Model

 


Fig. 4.22 RC model for determining $t_{PHL}(Z)$ and $t_{PLH}(F)$.

RC Model

 


Fig. 4.23 RC model for determining $t_{PHL}(F)$ and $t_{PLH}(Z)$.

Transistor Sizing

 


Fig. 4.24 Sizing result of a 4-input NAND gate.

Transistor Sizing

 


Fig. 4.25 Sizing result of Example 4.5.

Driving Identical Inverter

 


Fig. 4.26 Minimum size inverter driving another identical size inverter.

Driving Identical Inverter

 


Fig. 4.27 Another example of an inverter driving an identical size inverter.

Driving Identical Inverter

 


Fig. 4.28 Another example of an inverter driving an identical size inverter.

Buffer

 


Fig. 4.29 1× inverter driving a 10× inverter.

Buffer

 


Fig. 4.30 2× inverter driving a 10× inverter.

Buffer

 


Fig. 4.31 1× inverter driving two 10× inverters.

Buffer

 


Fig. 4.32 Non-inverting buffer driving a large load.

Buffer

 


Fig. 4.33 Replacing a large load with a $(C_L/C_{in})^x$ inverter.

Buffer

 


Fig. 4.34 Replacing the second inverter with a 100× inverter.

Driving Large Load

 


Fig. 4.35 Chain of inverter stages driving a large load.

Charging Load

 


Fig. 4.36 Charging a load capacitance through a pMOS transistor.

Parasitic Bipolar Transistors

 


Fig. 4.37 Parasitic bipolar transistors in a CMOS structure.

Parasitic Transistors

 


Fig. 4.38 Parasitic transistors of a CMOS logic.