
Chapter 8

Chip Design

Datapaht and Control

 


Fig. 8.1 Relationship between datapath and control units.

Finite-State Machine Controlled Datapath

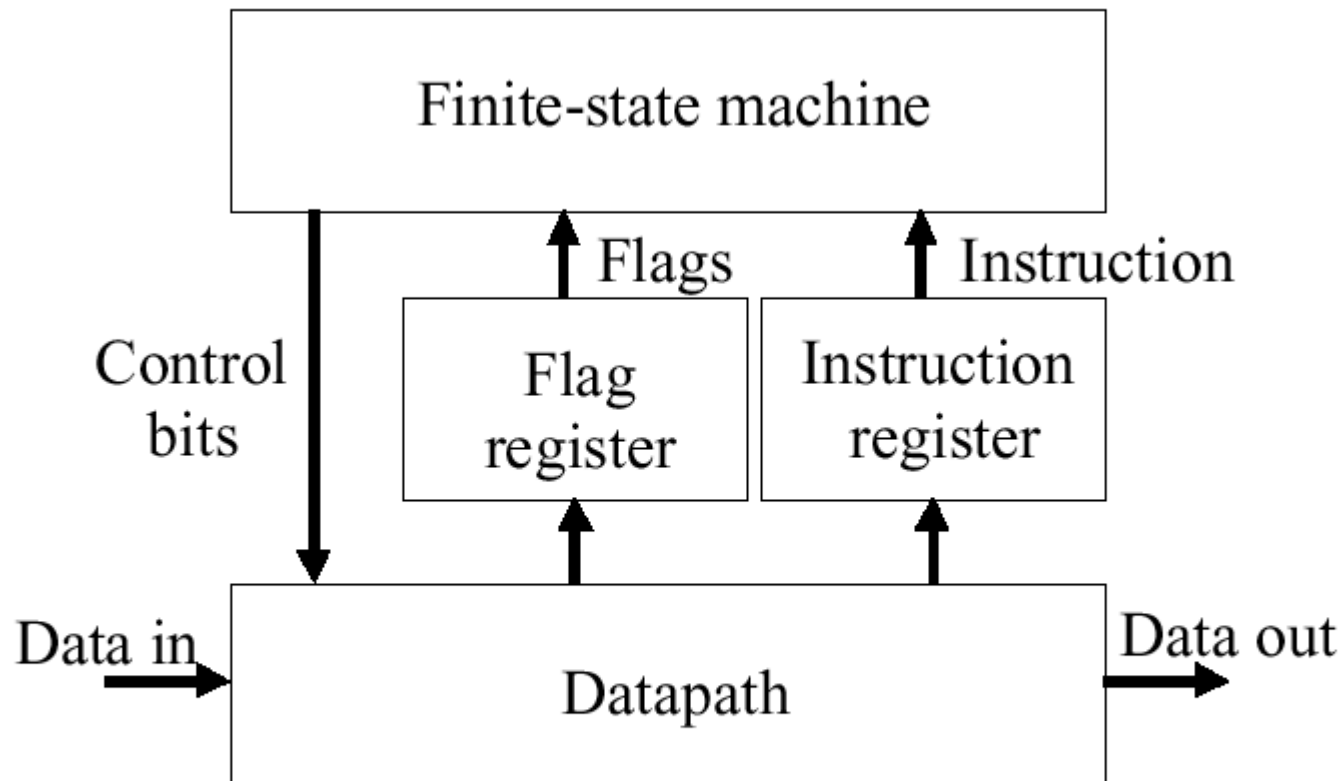


Fig. 8.2 Datapath controlled by a finite-state machine control unit.

Microprogrammed Datapath

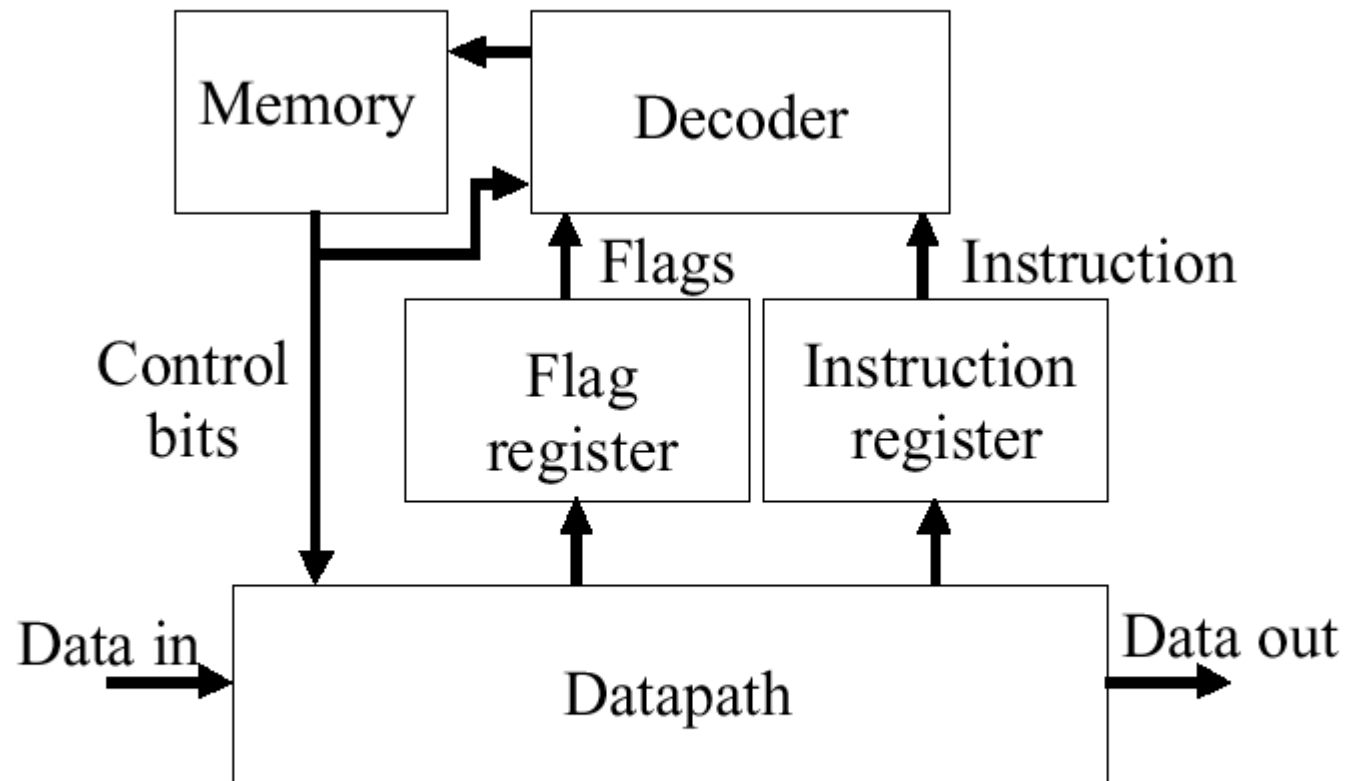


Fig. 8.3 Datapath controlled by a microprogrammed control unit.

SM and Memory

 


Fig. 8.4 Relationship between SM and a memory system.

SM Datapath

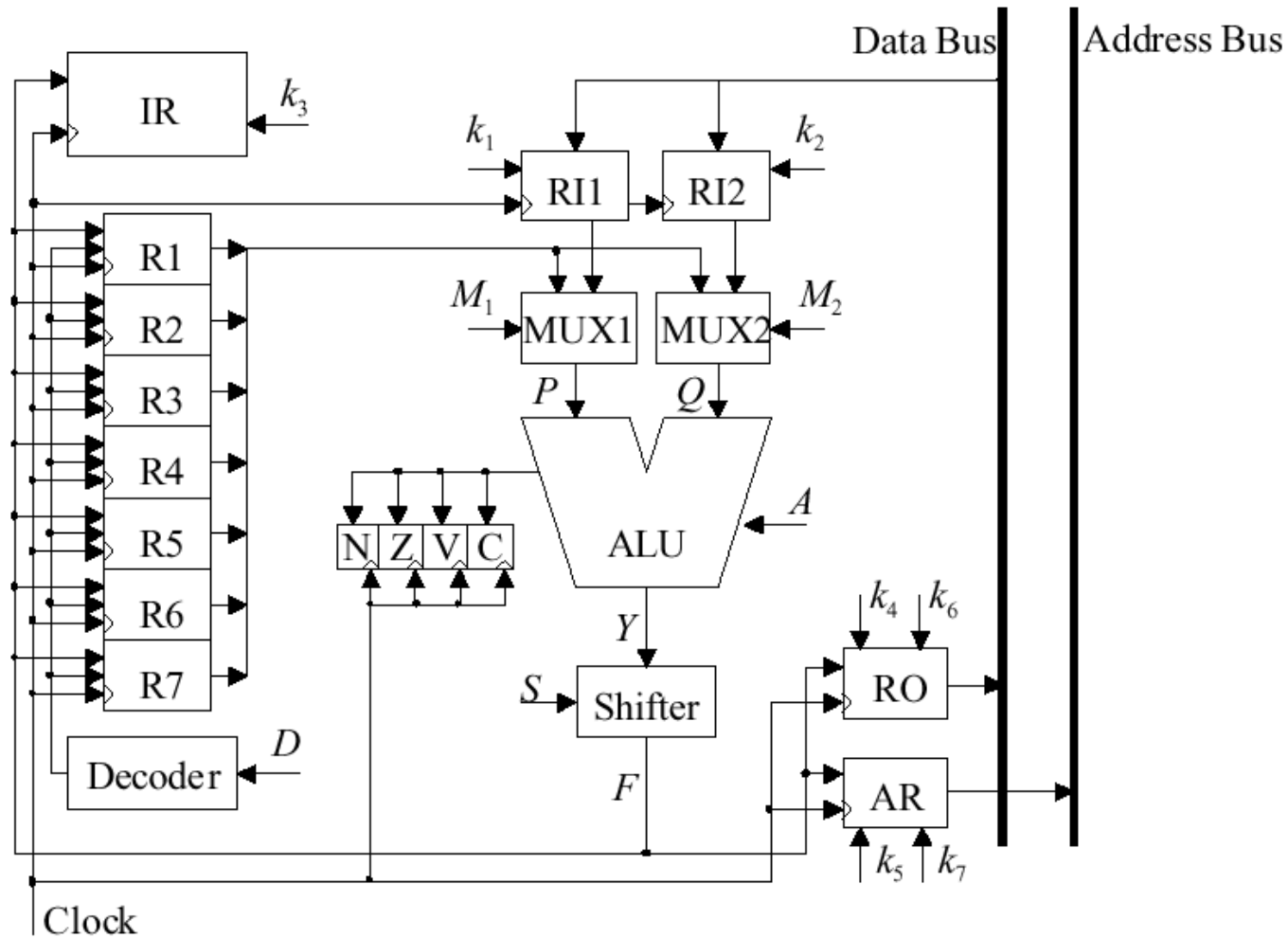


Fig. 8.5 Example SM datapath.

Control Signals

Code	A	M_1	M_2	S	D
000	$Y = P$	R11 selected	R12 selected	Bypass	
001	$Y = P + Q$	R1 selected	R1 selected	Logical Shift left ²	R1 loaded
010	$Y = P + 1$	R2 selected	R2 selected	Logical Shift right	R2 loaded
011	$Y = P - Q$	R3 selected	R3 selected	Output = 0	R3 loaded
100	$Y = \bar{P}$	R4 selected	R4 selected	Arithmetic Shift Left	R4 loaded
101	$Y = P \wedge Q$	R5 selected	R5 selected	Arithmetic Shift Right	R5 loaded
110	$Y = P \vee Q$	R6 selected	R6 selected	Rotate Left	R6 loaded
111	$Y = P \oplus Q$	R7 selected	R7 selected	Rotate Right	R7 loaded

Fig. 8.6 Control signals for ALU, MUX1, MUX2, shifter, and decoder.

Datapath Operations

Operation	A	M_1	M_2	S	D	$k_1k_2k_3k_4k_5k_6k_7$
$R1 \leftarrow R2 - R3$	011	010	011	000	001	0000000
$R2 \leftarrow \text{Shift right (R5)}$	000	101	-	010	010	0000000
$AR \leftarrow R7$	000	111	-	000	000	0000100
Memory $\leftarrow AR$	-	-	-	-	000	0000001

Fig. 8.7 Datapath operation examples.

ALU Bit Slice

 


Fig. 8.8 A bit slice of the ALU.

Shift Register

 


Fig. 8.9 Partial implementation of the shift register.

Instruction Format

 


Fig. 8.10 Instruction format.

Addressing Modes

Bits 10, 9	Addressing Mode	Address Calculation
00	(Rx)	Address = Rx
01	$m(Rx)$	Address = $m + Rx$
10	(Rx)[Ri]	Address = $Rx + Ri$
11	constant	Address = PC + 1

Fig. 8.11 Addressing modes.

Control Unit

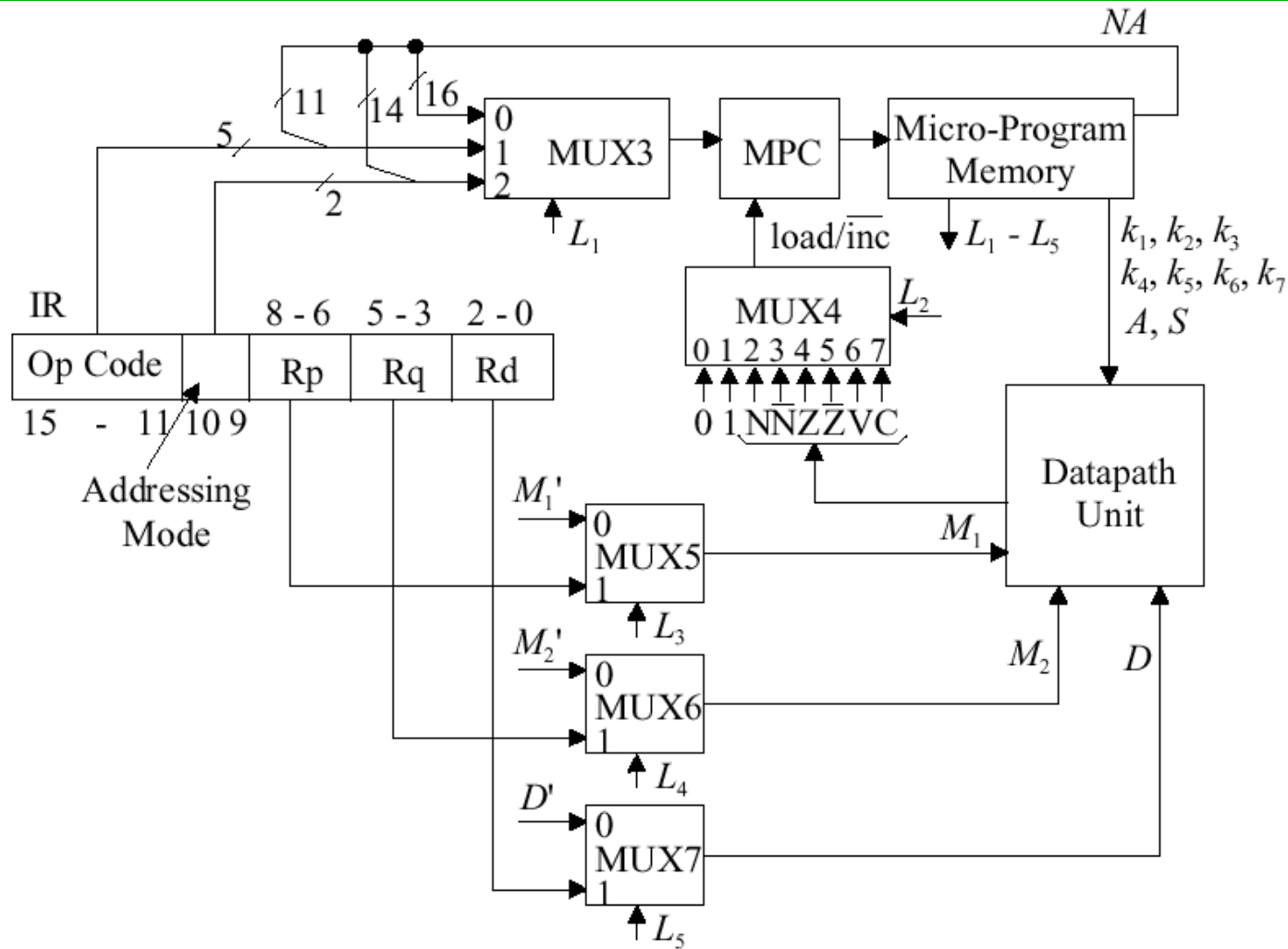


Fig. 8.12 Control unit of SM.

Microprogramming

	MPC Address	L_1	L_2	L_3	L_4	L_5	M_1'	M_2'	D'	NA	A	S	k_J-k_7
Instruction fetch:													
$AR \leftarrow R7$	0000	-	0	0	-	0	7	-	0	-	0	0	0000100
$BUS \leftarrow AR; R7 \leftarrow R7 + 1$	0001	-	0	0	-	0	7	-	7	-	2	0	0000001
$RI1 \leftarrow BUS$	0002	-	0	-	-	0	-	-	0	-	-	-	1000000
$IR \leftarrow RI1$	0003	-	0	0	-	0	0	-	0	-	0	0	0010000
Interpretation:													
determine next address	0004	1	1	-	-	0	-	-	0	0100	-	-	0000000
....													
LOAD:													
addressing modes	0100	2	1	-	-	0	-	-	0	0200	-	-	0000000
(other instructions)...												
Mode 00:	0200	0	1	-	-	0	-	-	0	0204	-	-	0000000
Mode 01:	0201	0	1	-	-	0	-	-	0	0208	-	-	0000000
Mode 10:	0202	0	1	-	-	0	-	-	0	020C	-	-	0000000
Mode 11:	0203	0	1	-	-	0	-	-	0	020D	-	-	0000000
(Rx)													
$AR \leftarrow Rx$	0204	-	0	1	-	0	-	-	0	-	0	0	0000100
$BUS \leftarrow AR$	0205	-	0	-	-	0	-	-	0	-	-	-	0000001
$RI1 \leftarrow BUS$	0206	-	0	-	-	0	-	-	0	-	-	-	1000000
$Rd \leftarrow RI1$	0207	0	1	0	-	1	0	-	-	0000	0	0	0000000
$m(Rx)$													
$AR \leftarrow R7$	0208	-	0	0	-	0	7	-	0	-	0	0	0000100
$BUS \leftarrow AR; R7 \leftarrow R7 + 1$	0209	-	0	0	-	0	7	-	7	-	2	0	0000001
$RI2 \leftarrow BUS$	020A	-	0	-	-	0	-	-	0	-	-	-	0100000
$AR \leftarrow RI2 + Rx$	020B	0	1	1	0	0	-	0	0	0205	1	0	0000100
$(Rx)[Ri]$													
$AR \leftarrow Ri + Rx$	020C	0	1	1	1	0	-	-	0	0205	1	0	0000100
constant													
$AR \leftarrow R7$	020D	-	0	0	-	0	7	-	0	-	0	0	0000100
$BUS \leftarrow AR; R7 \leftarrow R7 + 1$	020E	0	1	0	-	0	7	-	7	0206	2	0	0000001
...												

Fig. 8.13 Microprogramming example.

FPGA Floorplan

 


Fig. 8.14 General floorplan of an FPGA.

CLB

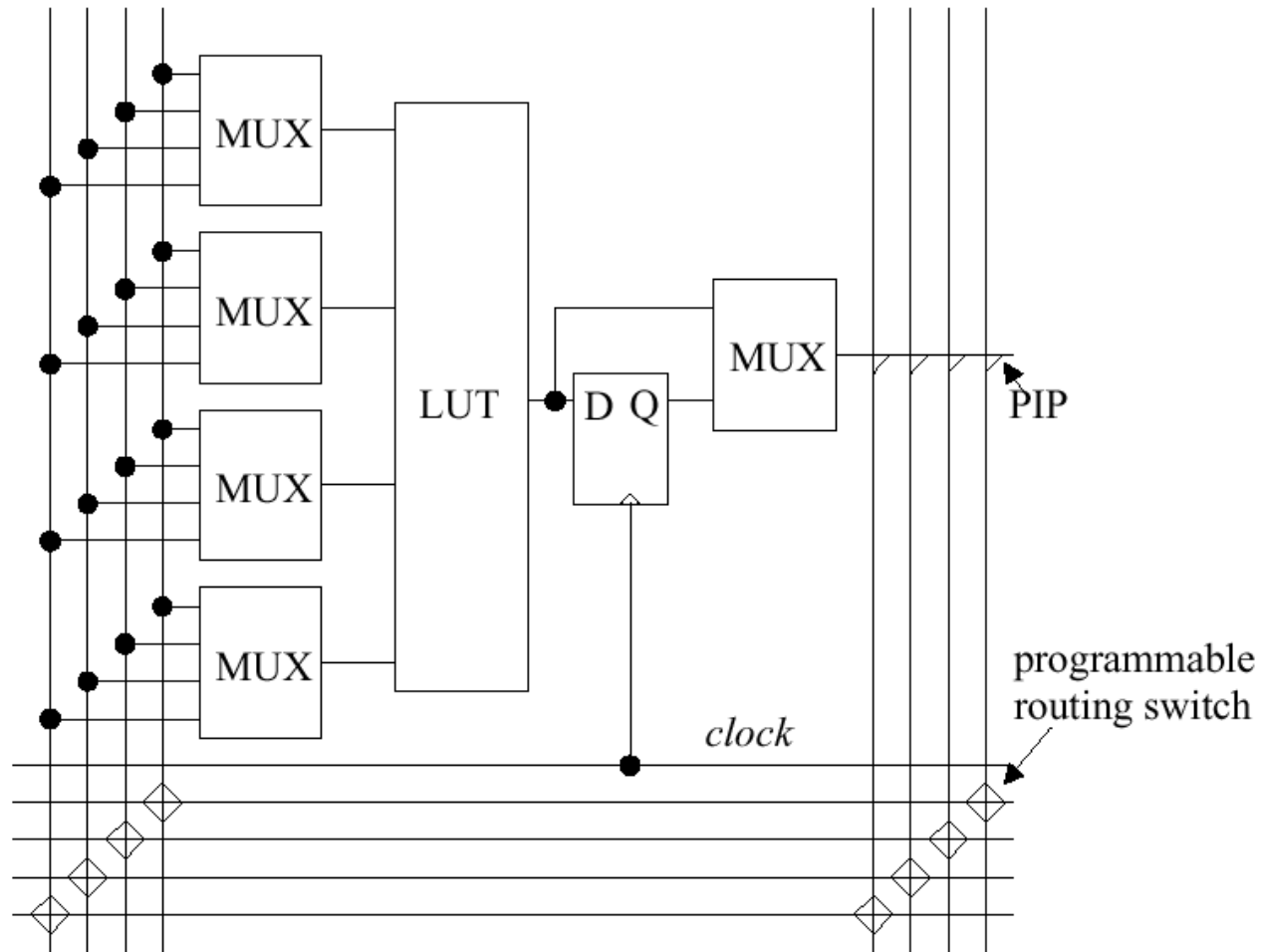


Fig. 8.15 Block diagram of CLB and its relationship with the routing resource.

Programmable Routing Switch

 


Fig. 8.16 Programmable routing switch.